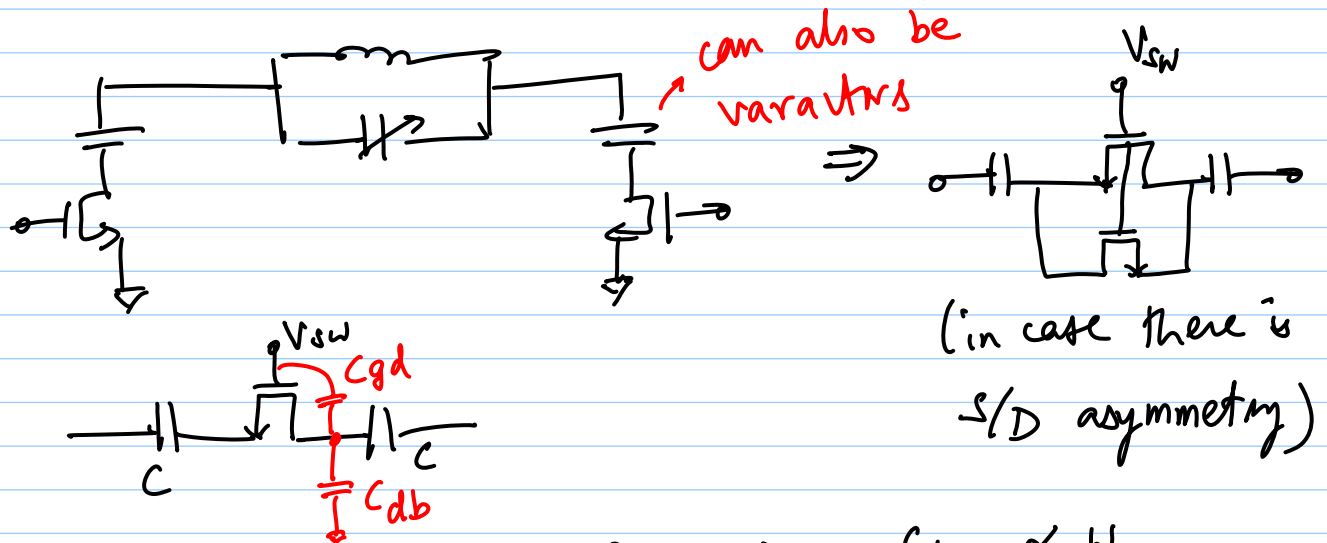


# Lecture 23: VCO Design (cont.)



$$C_{\max} = C \quad (V_{sw} = \text{ON})$$

$$C_{\min} = C \text{ series } (C_{gd} + C_{db})$$



$$\approx C_{gd} + C_{db} \quad (V_{sw} = \text{OFF})$$

$$C_{\text{par.}} \propto W$$



$$Q \propto W$$

⇒ trade-off between Q & Tuning range

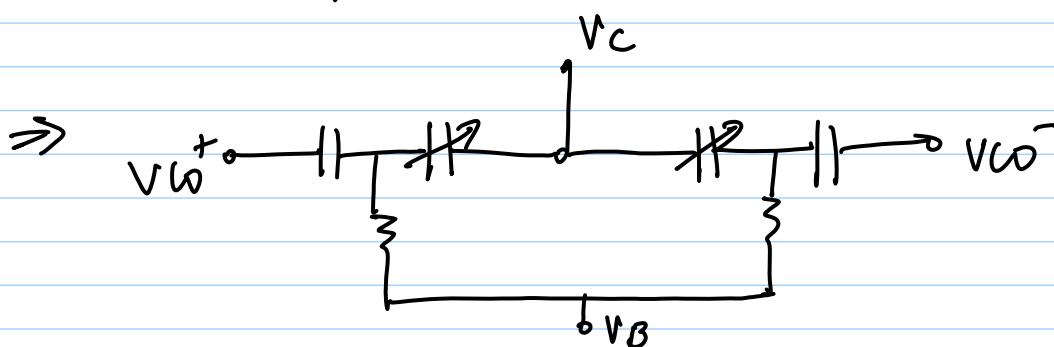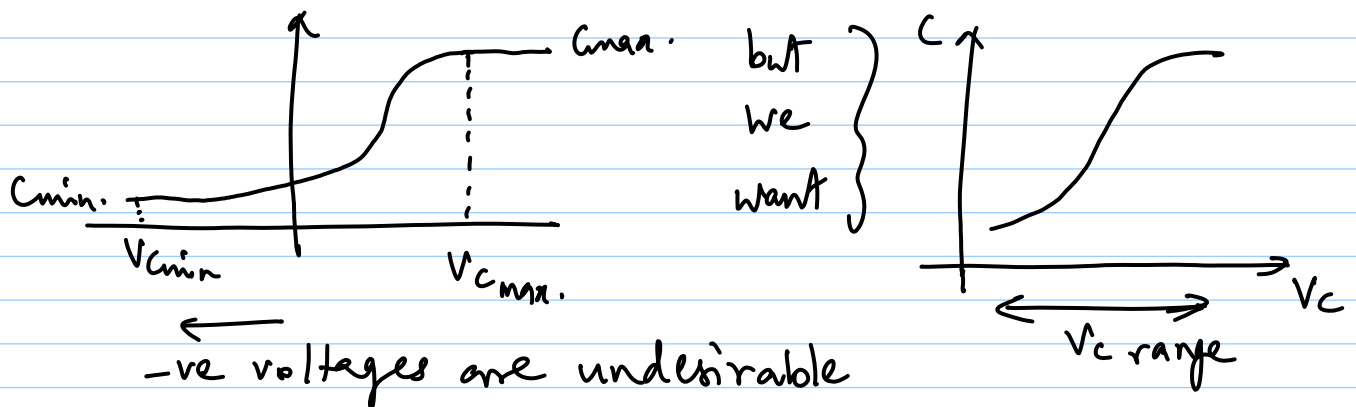\* Varactor may require re-biasing  
e.g. from  $\Delta V = (V_{DD} - V_C)$  to  $(V_B - V_C)$



\* differential Tuning also possible

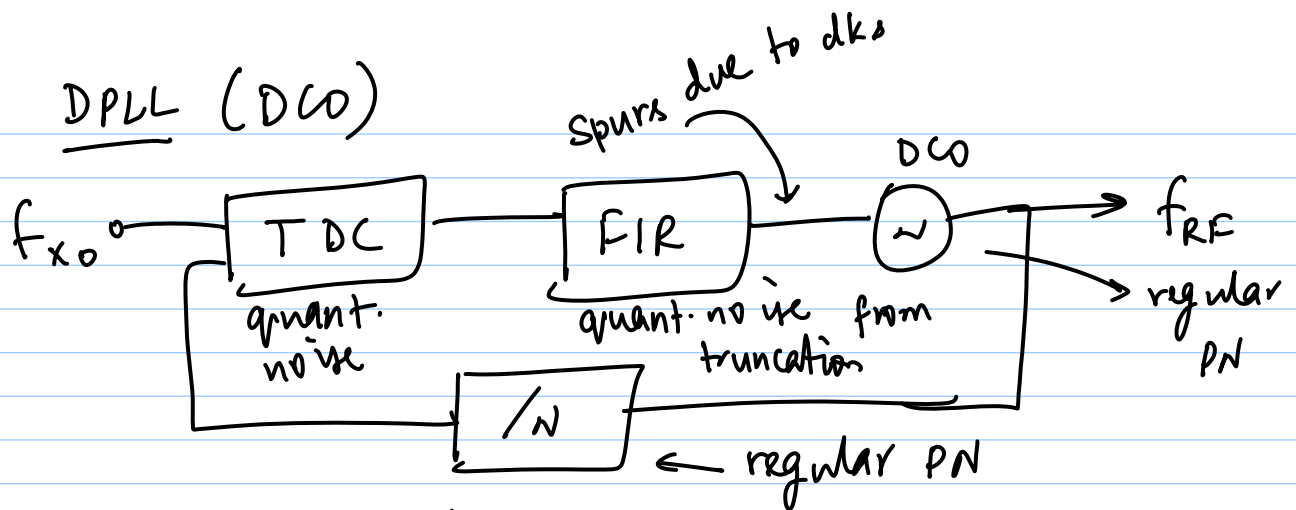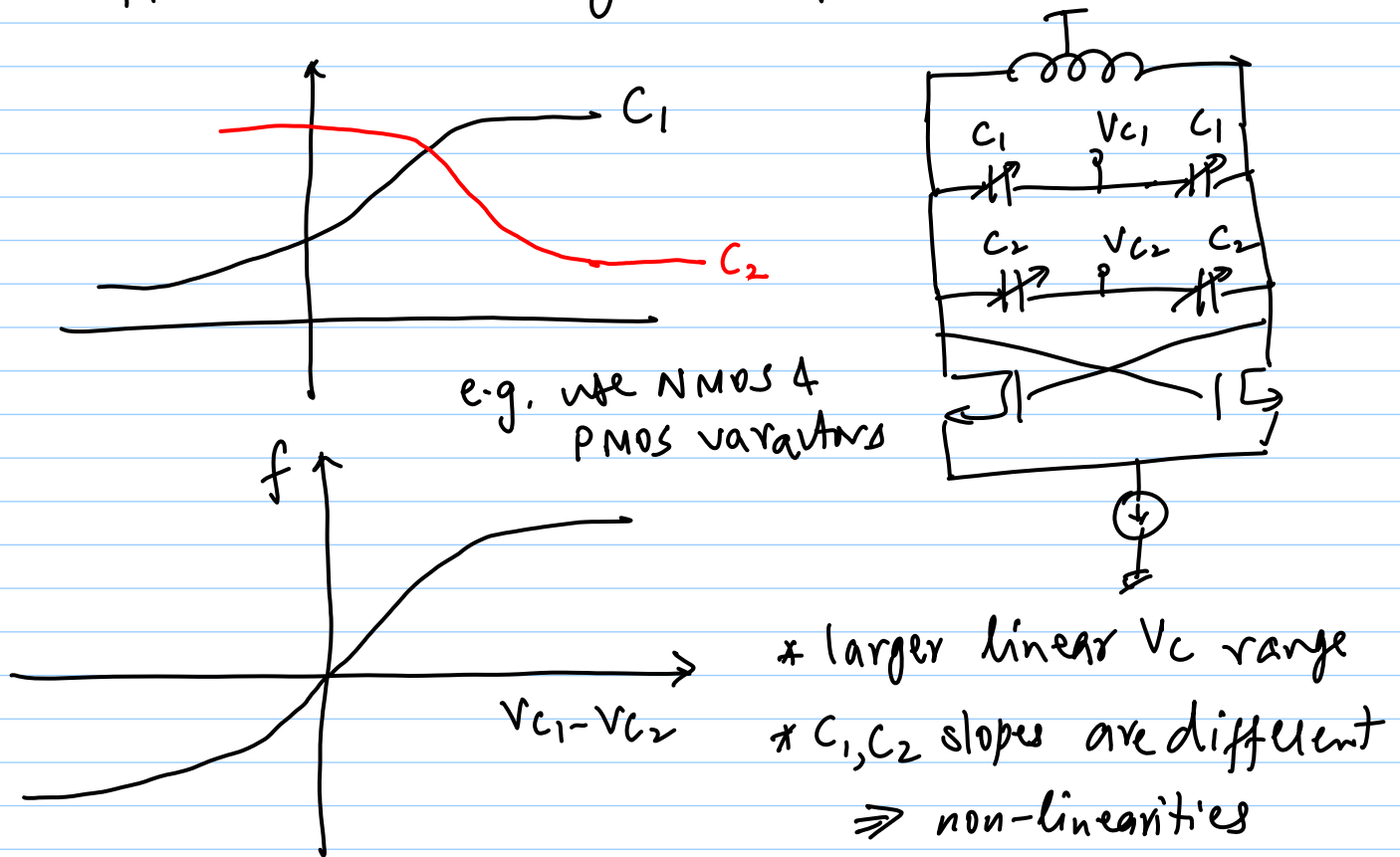

\* No analog tuning

\*  $f_{RF}$  needs very fine tuning


$\Rightarrow$  extremely small switchable  $C$  needed

e.g. 2kHz resolution @ 3.6GHz

$$C_{\text{tank}} = 4.5 \text{ pF}, L = 0.5 \text{ nH} \Rightarrow \Delta C = 5 \text{ aF} \quad (5 \times 10^{-18} \text{ F})$$

## Tail current filtering

\* popular technique, many variations

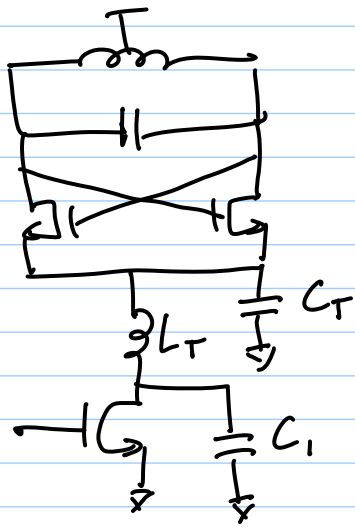

\* resonate  $L_T, C_T$  @  $2\omega_0$

→ high impedance @  $2\omega_0$


→ filters out noise folding down from  $2\omega_0$

\*  $C_1 = \text{large}$


→ filters out bias noise

\* extra  $L_T$  needed

## Voltage Regulator

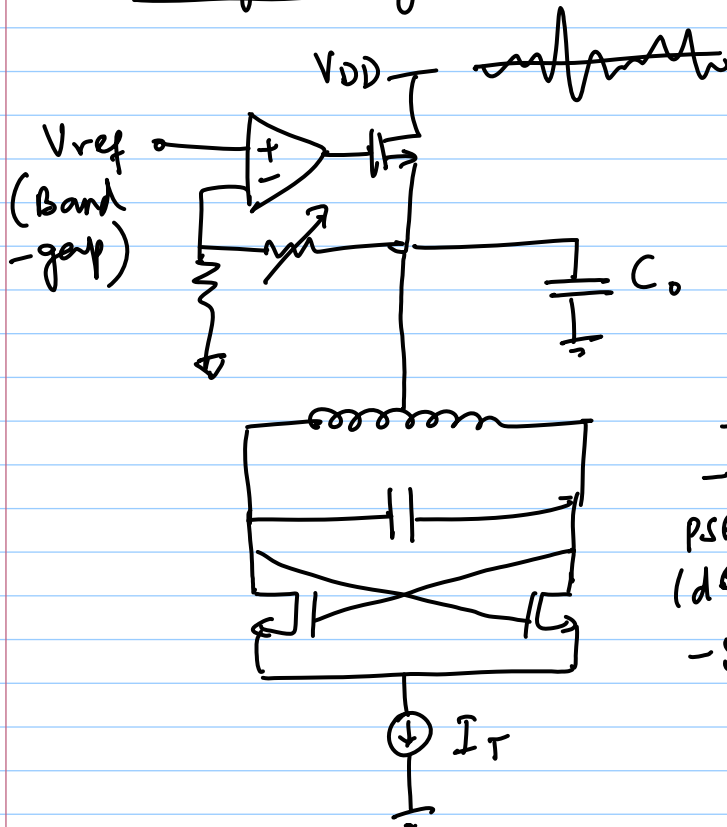


DC-DC converter has large noise, spurs

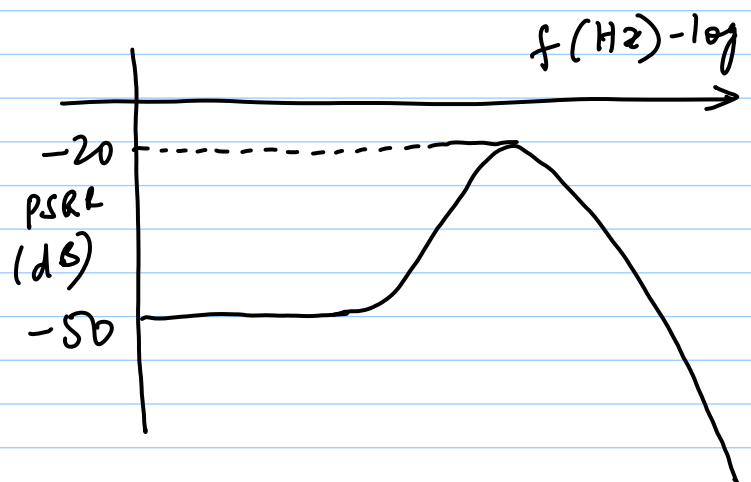

- \* Ensure regulator does not deteriorate PN (i.e. VCO - regulator co-design)
- \* Regulator power consumption must be kept low


Buffers - several configs possible

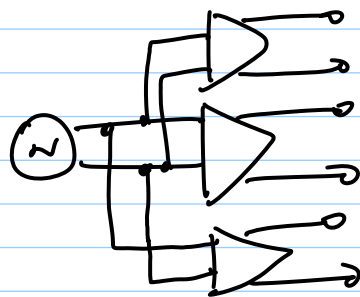


3 sets of outputs

- \* extra cap loading on VCO
- ⇒ tuning range reduced

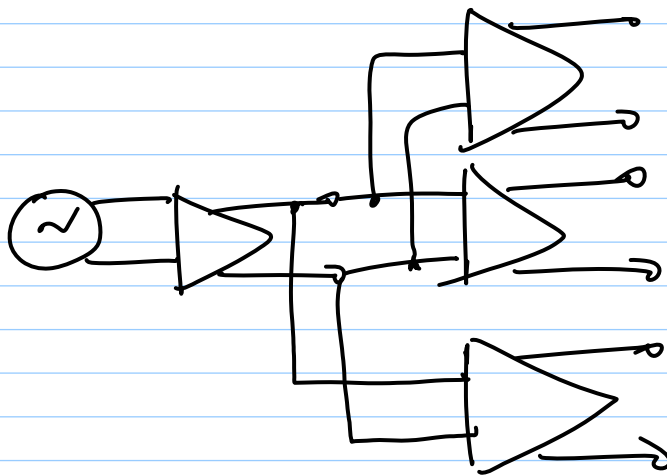very long routings or many in parallel  
⇒ use 2-stage



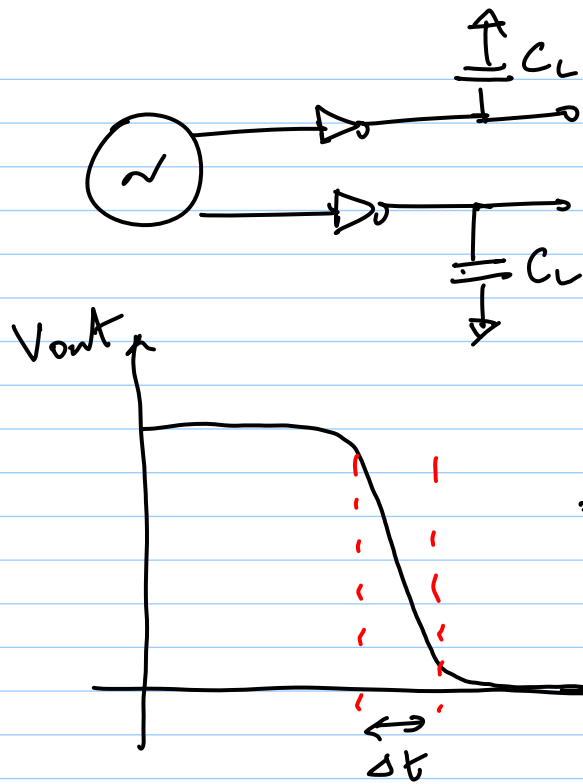- \* also reduces kickback from load driving (e.g. dividers)




- \*  $\phi$  sends - differential
- \* low - noise
- \*  $0 - V_{DD}$  outputs


(dividers are often digital)

\* inverter is most sensitive to noise during  $\Delta t$

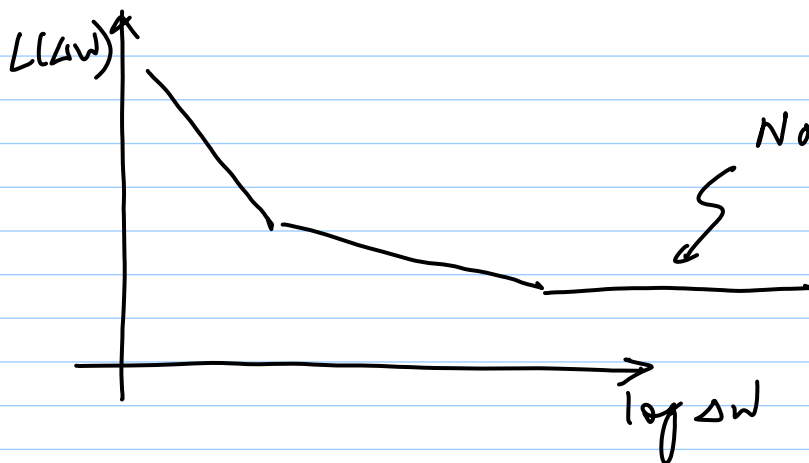
large  $C_L$  + narrow  $\Delta t \Rightarrow$  large inverters  
 $\Rightarrow$  high  $P_{dis}$ .



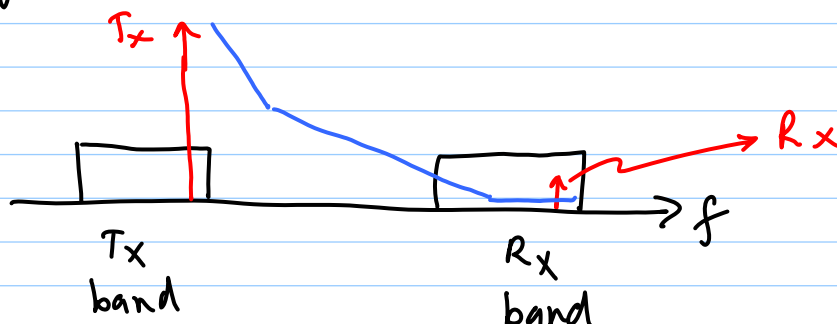
e.g. WCDMA (duplex,  $R_x$ ,  $T_x$  on at same time)



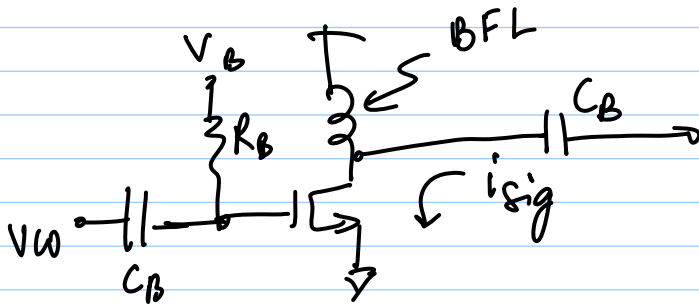high-freq. vcos: may need "open-drain" buffers



Effect of freq. division on PN

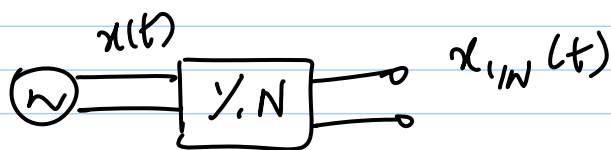

\* freq. & phase have a linear relationship

$$f \rightarrow f/N \Rightarrow \phi = \phi/N$$


$$x(t) = A \cos(\omega_0 t + \phi_n(t))$$

$$x_{1/N}(t) = A \cos\left(\frac{\omega_0}{N} t + \frac{\phi_n(t)}{N}\right)$$

$\Rightarrow$  PN magnitude at a given offset  $\rightarrow 1/N$

$\Rightarrow$  PN power  $\rightarrow 1/N^2$  { narrowband FM approx. }

## Bipolar VCOs

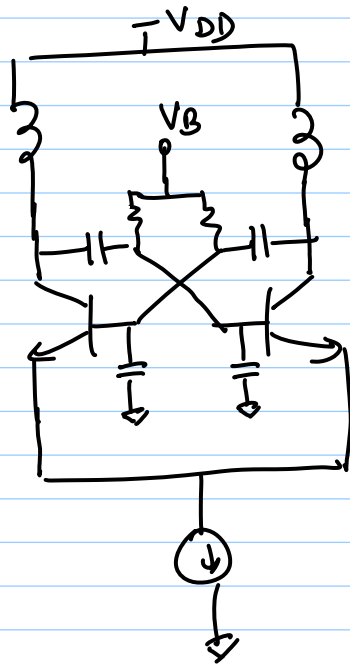

\* bipolar  $V_{BE} \sim 0.7V$

→ cap. divider allows larger swings @ o/p

\* feedback also possible using Xfmrs.

## VCO Design

- 1) Maximise Tank Q (i.e. highest  $R_p$ )
- 2) Maximise output swing, but don't saturate VCO {choose  $I_T$  carefully}
- 3) Startup gain of  $\sim 2-3$
- 4) Use minimum lengths to maximise tuning range (but keep  $1/f^3$  noise in mind)

5)  $R_p = W_0 L Q$  &  $V_0 = \frac{2}{\pi} I_T R_p$

$\Rightarrow$  minimize  $L$  &  $Q$  at the same time  
for min-  $P_N$  & min  $P_{Dis}$

6) Choose between

NMOS-only

PMOS-only

Complementary

Colpitts (differential)

Hybrid structures