
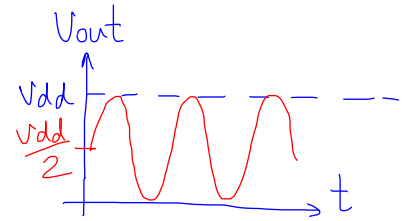


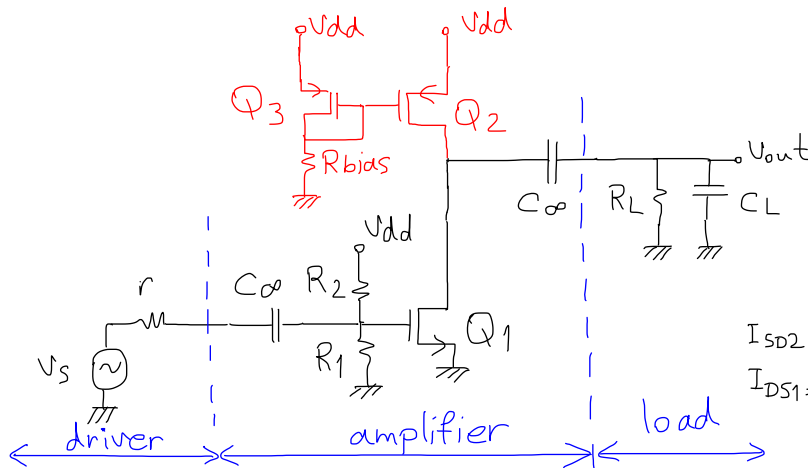* Common Source Amplifier parameters using indirect methods :




$$I_{SD2} = \frac{1}{2} \mu_p C_{ox} \frac{W_2}{L_2} (V_{SG2} - V_{th})^2 [1 + \lambda_p (V_{SD2})]$$

$$I_{DS1} = \frac{1}{2} \mu_n C_{ox} \frac{W_1}{L_1} (V_{GS1} - V_{th})^2 [1 + \lambda_n (V_{DS1})]$$


$$V_{SD2} + V_{DS1} = V_{DD}$$

$$V_{SD2} = V_{DS1} = \frac{V_{DD}}{2}$$

DC

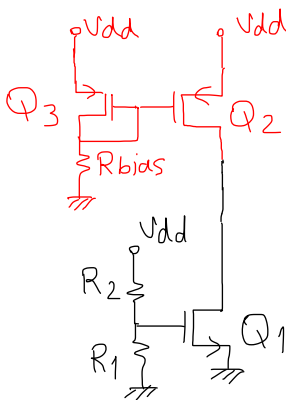


AC

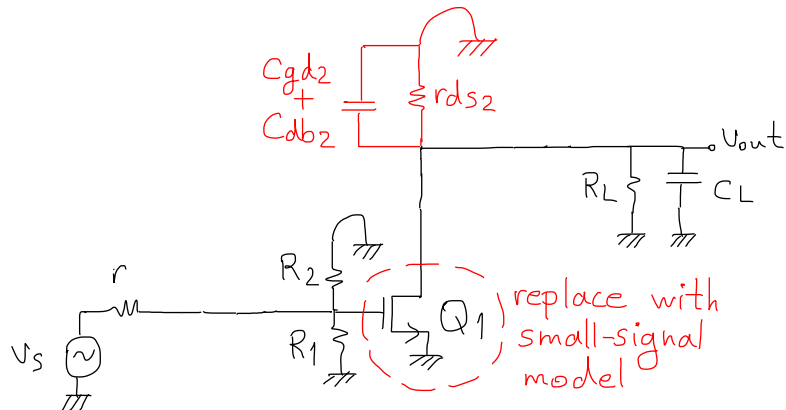

- find {
1. operating points (saturation, triode)
 2. small-signal parameters (g_m , r_{ds})


small-signal model

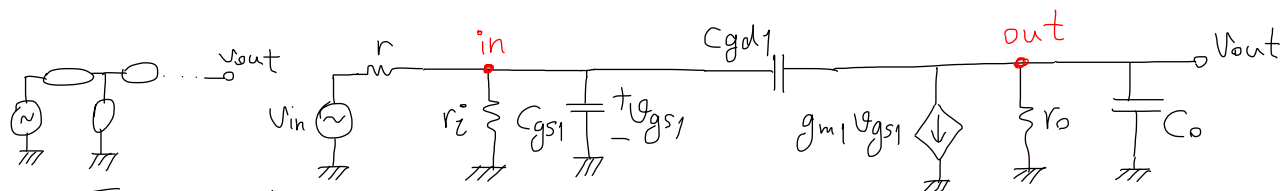

TI-arrayed

- find {
1. voltage gain
 2. poles, zeros
 3. input/output resistors

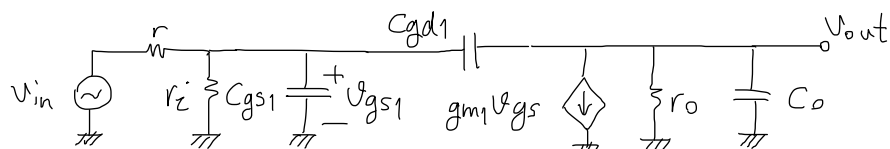* Common Source Amplifier parameters using indirect methods :




(mid-range)
* Find low-freq gain

→ To find A_{v0}


→ open all capacitors

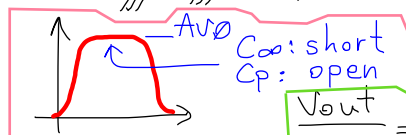→ find $\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = A_{v0}$ using KCL(in), KCL(out)




$$\frac{V_{out}}{V_{in}} = A_{v0} \frac{(1 + j\frac{\omega}{\omega_z})}{(1 + j\frac{\omega}{\omega_{p1}})(1 + j\frac{\omega}{\omega_{p2}})}$$

(Direct Method)

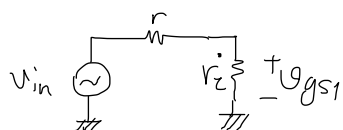
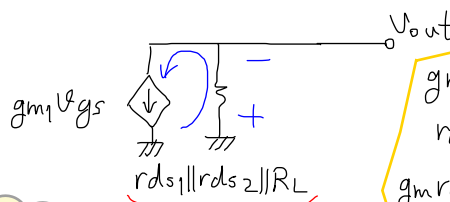
$$\begin{cases} V_{gs1} = V_{in} \frac{r_i}{r_i + r} \\ V_{out} = -g_{m1} V_{gs1} r_o \end{cases}$$



$$\Rightarrow \frac{V_{out}}{V_{in}} = A_{v0} = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = -g_{m1} (r_{ds1} \parallel r_{ds2} \parallel R_L) \frac{r_i}{r_i + r}$$

$$\begin{aligned} g_m &= \sqrt{2 I_{DQ} \mu_n C_{ox} \frac{W}{L}} \\ r_{ds} &= \frac{1}{\lambda I_{DQ}} \\ g_m r_{ds} &\propto \frac{1}{\sqrt{I_{DQ}}} \end{aligned}$$

* Find ω_z


→ To find zero, use output nulling method

→ find feedback component

→ if it is a capacitor, write KCL(out)

→ find conditions that make V_{out} zero

$$j\omega C_{gd1}(V_{gs1} - V_{out})$$

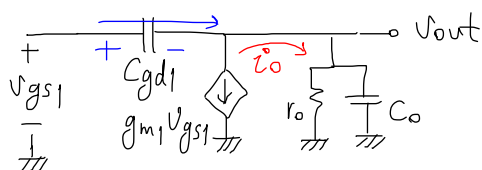


$$V_{out} = 0 \Rightarrow i_o = 0$$

$$KCL(out): i_o = j\omega C_{gd1}(V_{gs1} - V_{out}) - g_{m1} V_{gs1}$$

$$\Rightarrow 0 = (j\omega C_{gd1} - g_{m1}) V_{gs1} - j\omega C_{gd1} V_{out}$$



$$j\omega_z = \frac{g_{m1}}{C_{gd1}}$$

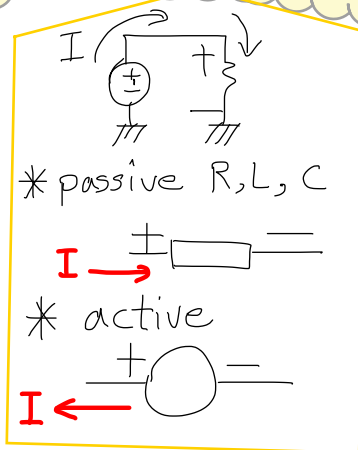


* Find ω_{p1}

→ To find ω_{p1} (first pole), use open circuit time constant method

- ↳ keep one of the capacitors C_i
 - ↳ open all other capacitors
 - ↳ find resistance R_i across C_i
 - ↳ repeat above steps for other capacitors
- $$\omega_{p1} = \frac{1}{\sum R_i C_i}$$

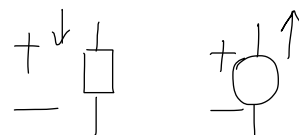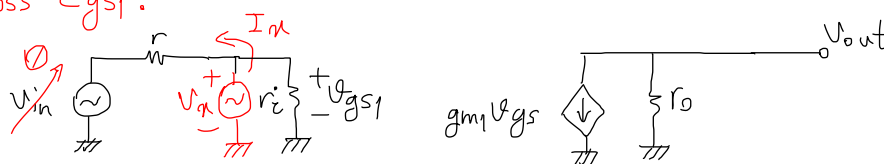* Across C_{gs1} :

$$R_n \text{ seen across } C_{gs1} : \frac{V_n}{I_n} = r \parallel r_i \Rightarrow \tau_1 = (r \parallel r_i) C_{gs1}$$

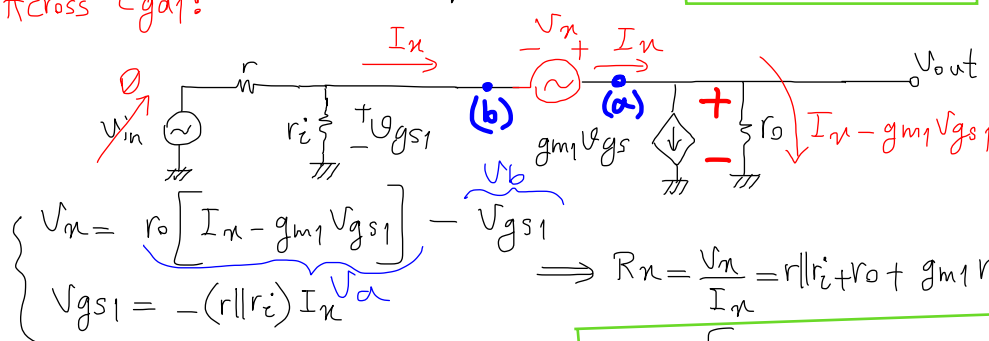* Across C_{gd1} :

$$\begin{cases} V_n = r_o [I_n - g_{m1} V_{gs1}] - V_{gs1} \\ V_{gs1} = -(r \parallel r_i) I_n \end{cases} \Rightarrow R_n = \frac{V_n}{I_n} = r \parallel r_i + r_o + g_{m1} r_o (r \parallel r_i)$$

$$\tau_2 = [r \parallel r_i + r_o + g_{m1} r_o (r \parallel r_i)] C_{gd1}$$

* Across C_o :


$$R_n = \frac{V_n}{I_n} = r_o = r_{ds1} \parallel r_{ds2} \parallel R_L$$

$$\tau_3 = (r_{ds1} \parallel r_{ds2} \parallel R_L) (C_{db1} + C_L + C_{gd2} + C_{db2})$$

$$\omega_{p1} = \frac{1}{\tau_1 + \tau_2 + \tau_3}$$

=> Finding the Resistance across C_{gs1} in more details :


$$V_n = V_a - V_b$$

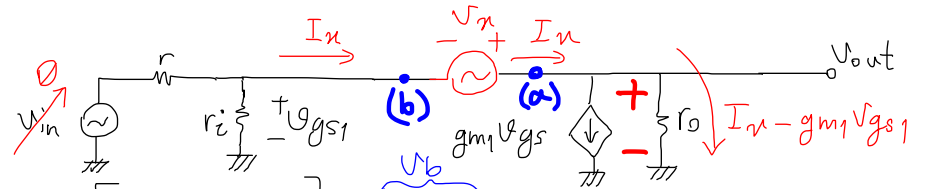

$$\begin{cases} V_n = r_o [I_n - g_{m1} V_{gs1}] - V_{gs1} \\ V_{gs1} = -(r \parallel r_i) I_n \end{cases} \Rightarrow R_n = \frac{V_n}{I_n} = r \parallel r_i + r_o + g_{m1} r_o (r \parallel r_i)$$


$$\tau_2 = [r \parallel r_i + r_o + g_{m1} r_o (r \parallel r_i)] C_{gd1}$$

$$V_n = V_b - V_a$$

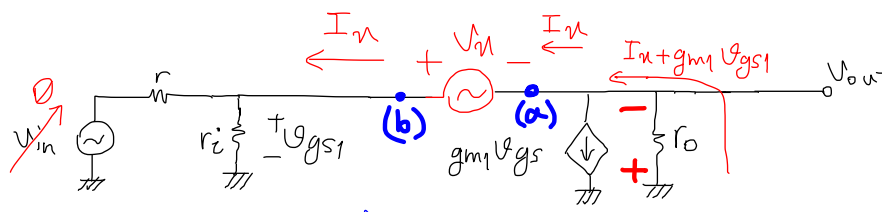

$$\begin{cases} V_n = V_{gs1} - (-r_o [I_n + g_{m1} V_{gs1}]) \\ V_{gs1} = I_n (r \parallel r_i) \end{cases}$$

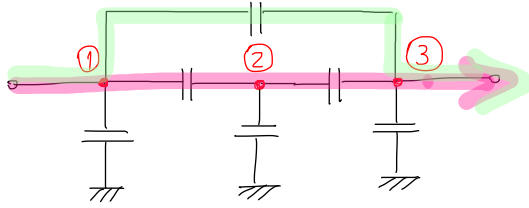* If we have multiple poles & zeros in the circuit:



$$Z_1 = C_{t1} \cdot R_{t1}$$

$$Z_1 < Z_2 < Z_3$$

$$\omega_{p1} = \frac{1}{Z_1 + Z_2 + Z_3}$$

because there are
two capacitive
paths from input
to output

$$\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = A_{v0} \frac{\left(1 + j\frac{\omega}{\omega_{z1}}\right)\left(1 + j\frac{\omega}{\omega_{z2}}\right)}{\left(1 + j\frac{\omega}{\omega_{p1}}\right)\left(1 + j\frac{\omega}{\omega_{p2}}\right)\left(1 + j\frac{\omega}{\omega_{p3}}\right)}$$

because circuit has
three nodes

$$\omega_{p1} < \omega_{p2} < \omega_{p3}$$