
EE230-02 RFIC II

Fall 2018


Lecture 6: LNA1

Prof. Sang-Soo Lee
sang-soo.lee@sjsu.edu
ENG-259


LNA General Considerations

- ☐ Noise Figure
- ☐ Gain
- ☐ Input Return Loss
- ☐ Stability
- ☐ Linearity
- ☐ Bandwidth
- ☐ Power Dissipation

Noise Review

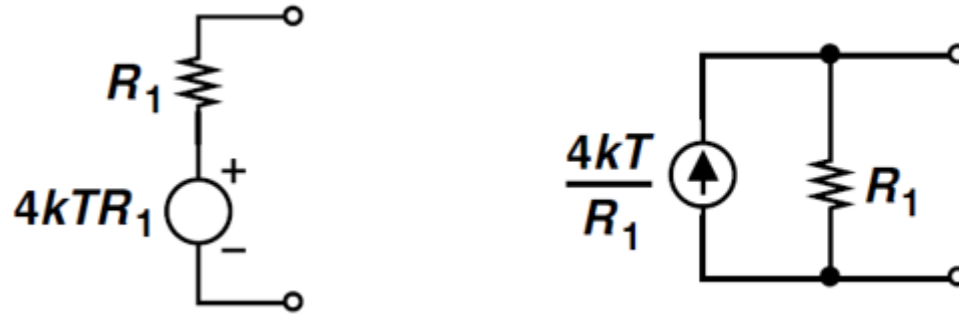

Resistor Noise

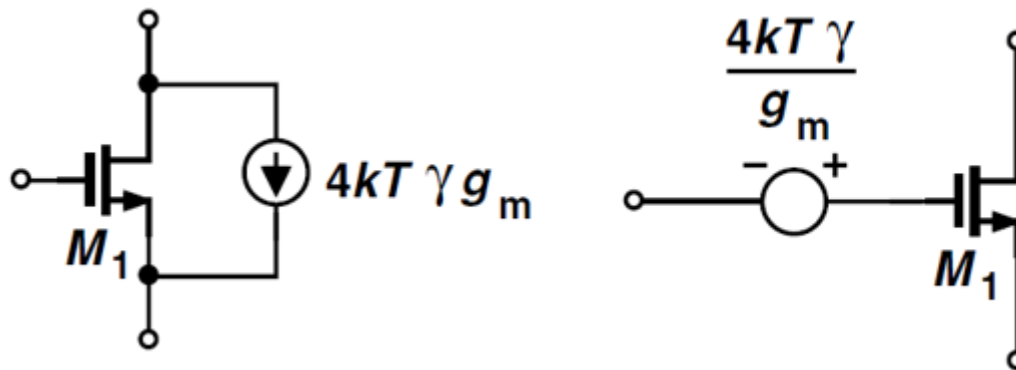


MOSFET Thermal Noise


$$\overline{V_n^2} = \frac{K}{WLC_{ox}} \frac{1}{f}$$

MOSFET 1/f Noise

Gate Resistance

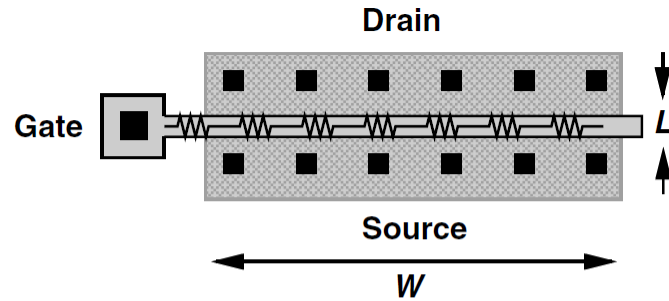


(a)

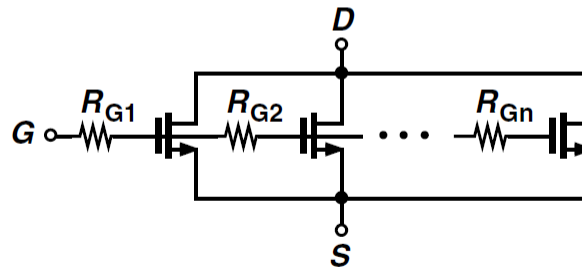

$$R_{G1} + R_{G2} + \dots + R_{Gn} = R_G$$

(b)

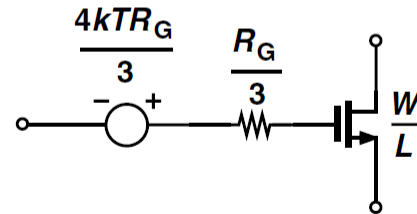


(c)

Design for

$$4kT \frac{R_G}{3} \ll \frac{4kT\gamma}{g_m}$$

Noise Figure

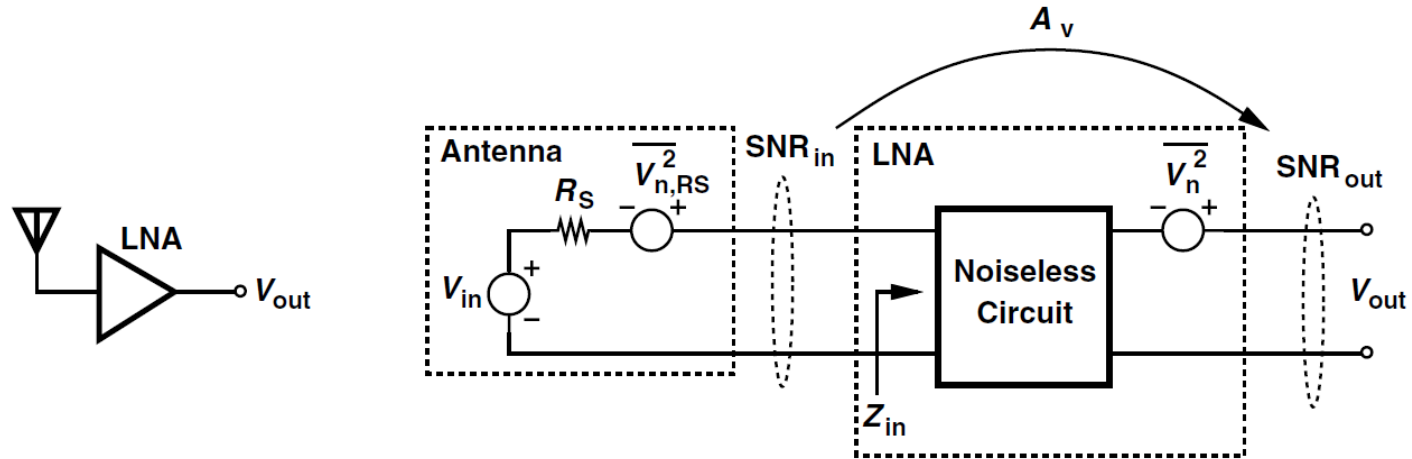


$$NF = \frac{SNR_{in}}{SNR_{out}} \quad SNR_{in} = \frac{|\alpha|^2 V_{in}^2}{|\alpha|^2 \overline{V_{RS}^2}} \quad SNR_{out} = \frac{V_{in}^2 |\alpha|^2 A_v^2}{\overline{V_{RS}^2} |\alpha|^2 A_v^2 + \overline{V_n^2}}$$

$$NF = \frac{V_{in}^2}{4kTR_S} \cdot \frac{\overline{V_{RS}^2} |\alpha|^2 A_v^2 + \overline{V_n^2}}{V_{in}^2 |\alpha|^2 A_v^2} = \frac{1}{4kTR_S} \cdot \frac{V_{n,out}^2}{A_0^2} = \frac{\text{Total Output Noise}}{\text{Output Noise due to Source}}$$

$$= \frac{\text{Noise due to Source} + \text{Noise due to Circuit}}{\text{Noise due to Source}} = 1 + \frac{\text{Noise due to Circuit}}{\text{Noise due to Source}}$$

Metal Resistance on NF

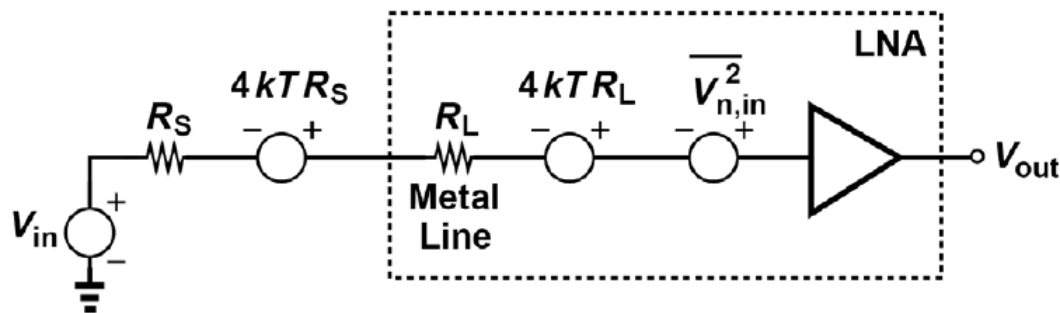A student lays out an LNA and connects its input to a pad through a metal line 200 μm long. In order to minimize the input capacitance, the student chooses a width of 0.5 μm for the line. Assuming a noise figure of 2 dB for the LNA and a sheet resistance of 40 m Ω/\square for the metal line, determine the overall noise figure.



$$\begin{aligned}
 NF_{\text{tot}} &= 1 + \frac{\overline{V_{n,in}^2} + 4kTR_L}{4kTR_S} \\
 &= 1 + \frac{\overline{V_{n,in}^2}}{4kTR_S} + \frac{R_L}{R_S} \\
 &= NF_{\text{LNA}} + \frac{R_L}{R_S},
 \end{aligned}$$


where NF_{LNA} denotes the noise figure of the LNA without the line resistance. Since $NF_{\text{LNA}} = 2 \text{ dB} \equiv 1.58$ and $R_L = (200/0.5) \times 40 \text{ m}\Omega/\square = 16 \Omega$, we have

$$NF_{\text{tot}} = 2.79 \text{ dB}$$

Noise Figure



➤ The noise figure of the LNA directly adds to that of the receiver.

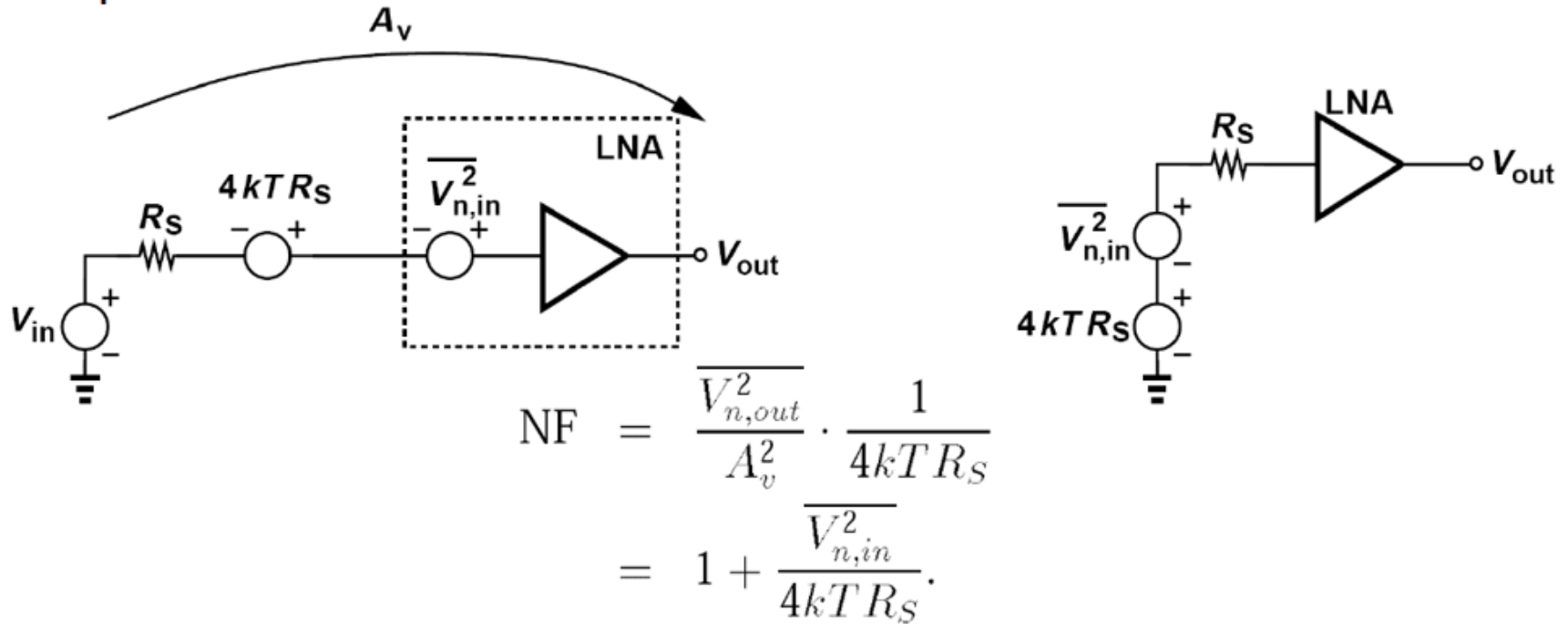It is expected that the LNA contributes 2 to 3 dB of noise figure. Consider the simple example shown below:



Noise Figure

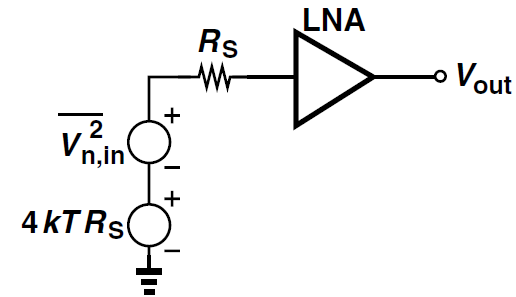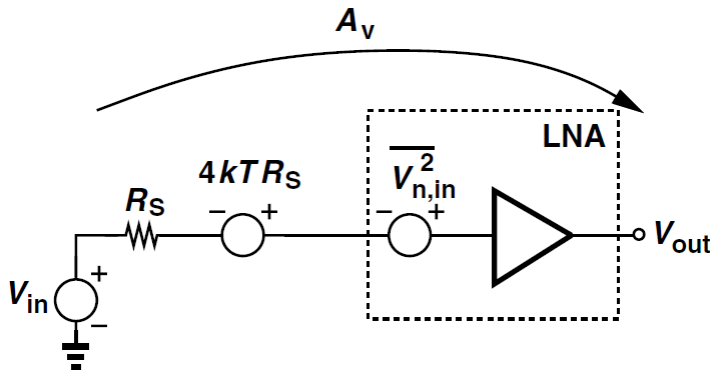How much is the noise voltage for the 2 dB NF?



$$\text{NF} = \frac{\overline{V_{n,out}^2}}{A_v^2} \cdot \frac{1}{4kTR_S}$$


$$= 1 + \frac{\overline{V_{n,in}^2}}{4kTR_S}$$

$$2 \text{ dB} = 1.58$$

$$\frac{\overline{V_{n,in}^2}}{4kTR_S} = 0.58, \quad R_S = 50\Omega$$

$$\Rightarrow \sqrt{\overline{V_{n,in}^2}} = 0.696 \text{ nV}/\sqrt{\text{Hz}}$$

Noise Figure Calculation Example

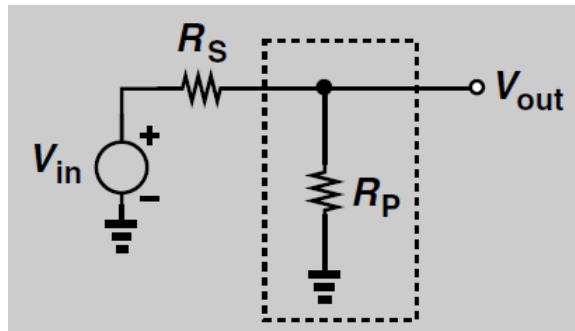

Total output noise

$$\overline{V_{n,out}^2} = 4kT (R_s || R_p)$$

Gain $A_v = \frac{V_{out}}{V_{in}} = \frac{R_p}{R_s + R_p}$


$$NF = \frac{\text{Total Output Noise}}{\text{Output Noise due to Source}}$$

$$= \frac{4kT (R_s || R_p)}{4kT R_s \cdot A_v^2} = \frac{\frac{R_s \cdot R_p}{R_s + R_p}}{R_s \cdot \left(\frac{R_p}{R_s + R_p} \right)^2} = \frac{R_s + R_p}{R_p} = 1 + \frac{R_s}{R_p}$$

The NF is therefore minimized by *maximizing* R_p .
Note that if $R_p = R_s$ to provide impedance matching, then the NF cannot be less than 3 dB.

Noise Figure Calculation Example

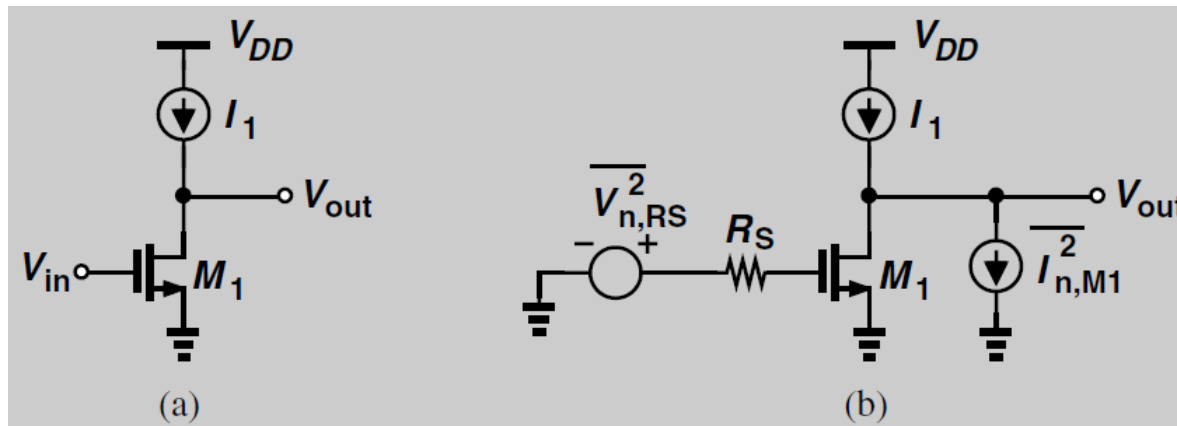
Determine the noise figure of the common-source stage shown below with a source impedance R_S . Neglect the capacitances and flicker noise of M_1 and assume I_1 is ideal.




$$\begin{aligned}
 NF &= \frac{\text{Total Output Noise}}{\text{Output Noise due to Source}} \\
 &= \frac{(4kT\gamma g_m)r_o^2 + 4kTR_s(g_mr_o)^2}{4kTR_s(g_mr_o)^2} = \frac{\gamma}{g_mR_s} + 1
 \end{aligned}$$

Gain of LNA

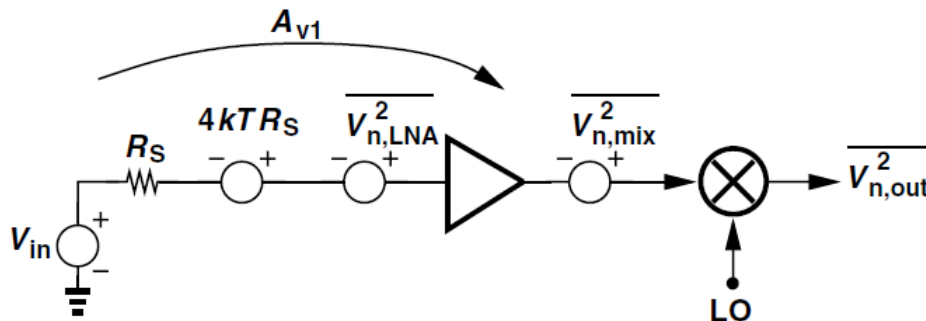- ❑ Must be large enough to minimize noise contributed by mixer
- ❑ Trade with IP3


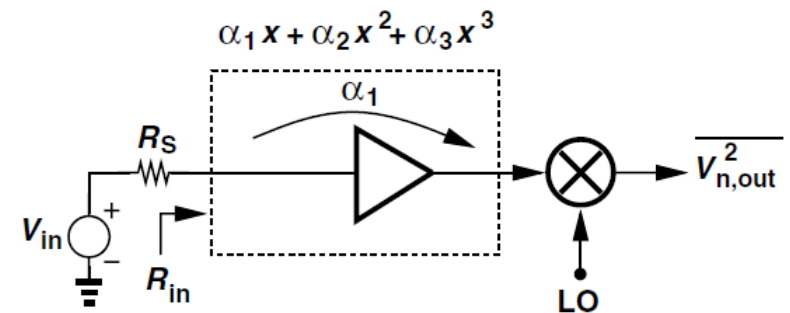
$$NF_{tot} = NF_1 + \frac{NF_2 - 1}{A_{P1}}$$



$$\frac{1}{IP_{3,tot}^2} = \frac{1}{IP_{3,LNA}^2} + \frac{\alpha_1^2}{IP_{3,mixer}^2}$$

Cascade IP3 Example


LNA

IP3 = -10 dBm

Gain = 20 dB

Mixer

IP3 = +4 dBm

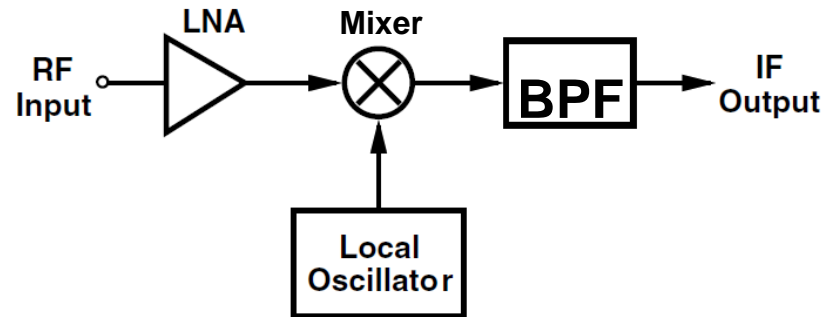

Which stage limits the IP3 of the cascade more?

$$\frac{1}{IP_{3,tot}^2} = \frac{1}{IP_{3,LNA}^2} + \frac{\alpha_1^2}{IP_{3,mixer}^2}$$

$$IP_{3,LNA} = -10 \text{ dBm}$$

$$\frac{IP_{3,Mixer}}{\alpha_1} = -16 \text{ dBm} \quad \leftarrow \text{Mixer limits the overall IP3 more.}$$

Input Return Loss

- The quality of the input match is expressed by the input “return loss,” defined as the reflected power divided by the incident power. For a source impedance of R_S , the return loss is given by:

$$\Gamma = \left| \frac{Z_{in} - R_S}{Z_{in} + R_S} \right|^2$$

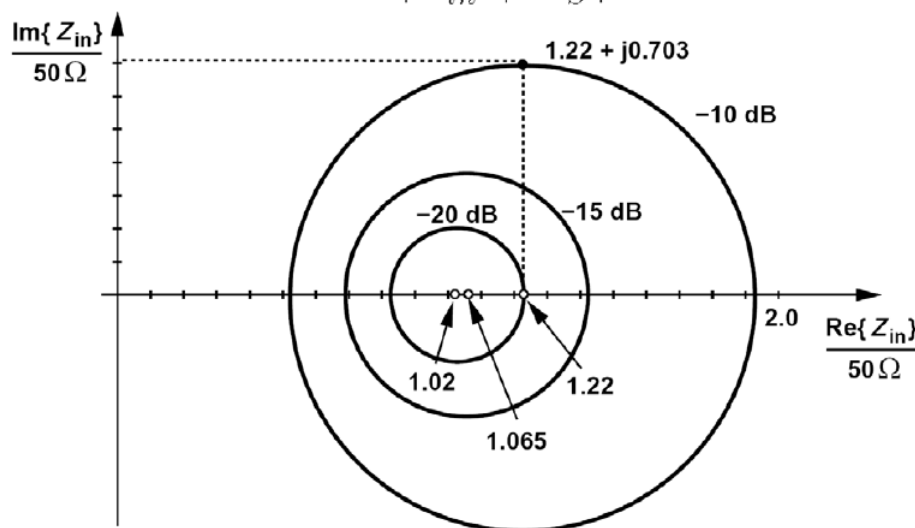


Figure above plots contours of constant Γ in the Z_{in} plane. Each contour is a circle with its center shown.

- An input return loss of -10 dB signifies that one tenth of the power is reflected
→ A typically acceptable value.
- In practice, a Γ of about -15 dB is targeted so as to allow margin for package parasitics, etc.

Stability

Stern Stability Factor

$$K = \frac{1 + |\Delta|^2 - |S_{11}|^2 - |S_{22}|^2}{2|S_{21}||S_{12}|}$$

$$\Delta = S_{11}S_{22} - S_{12}S_{21}$$

If $K > 1$ and $|\Delta| < 1$, then the circuit is unconditionally stable

- LNAs can be stabilized by maximizing their reverse isolation.
- A high reverse isolation is also necessary for suppressing the LO leakage to the input of the LNA.


Bandwidth

- The LNA must provide a relatively flat response for the frequency range of interest, preferably with less than 1 dB of gain variation.
- The LNA -3dB bandwidth must therefore be substantially larger than the actual band so that the roll-off at the edges remains below 1 dB.

An 802.11a LNA must achieve a -3-dB bandwidth from 5 GHz to 6 GHz. If the LNA incorporates a second-order LC tank as its load, what is the maximum allowable tank Q ?



Fractional bandwidth
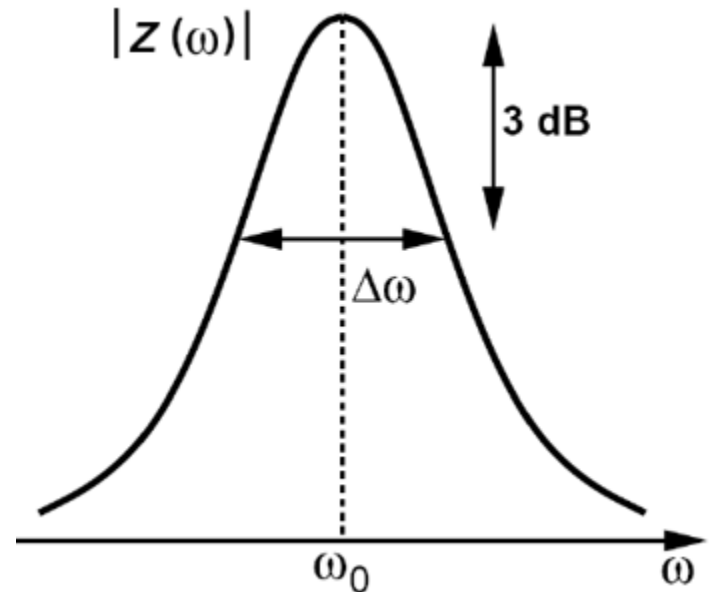
$$\frac{\Delta\omega}{\omega_0} = \frac{1G}{5.5G} = \frac{1}{5.5} = \frac{1}{Q}$$



Band Switching

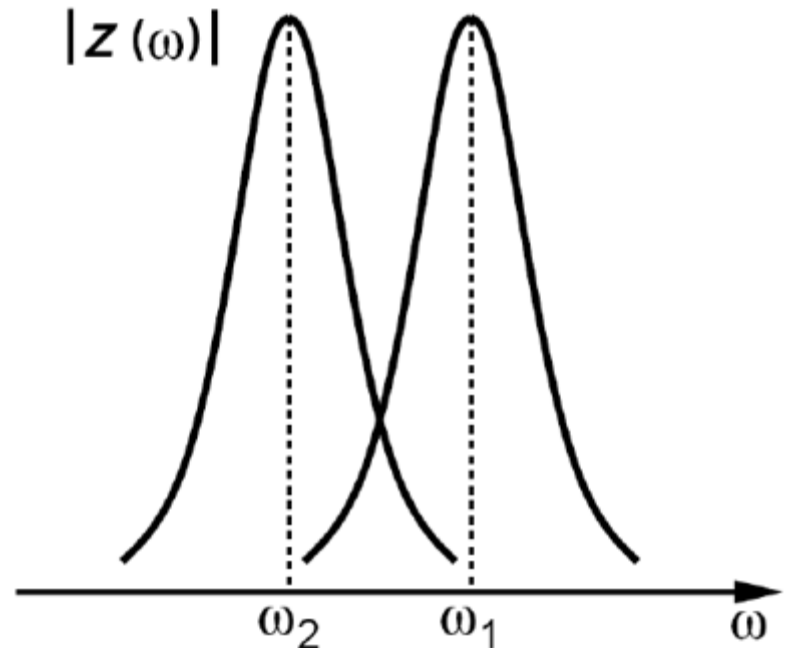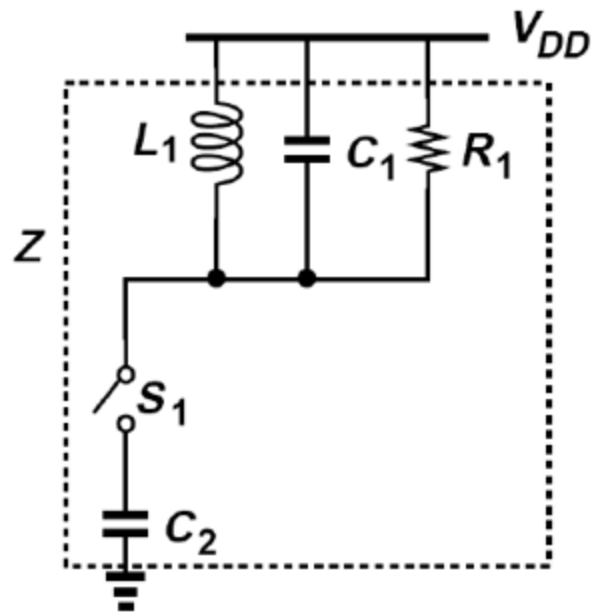LNA designs that must achieve a relatively large fractional bandwidth may employ a mechanism to *switch* the center frequency of operation.




LNA Topologies

Common-Source Stage with	Common-Gate Stage with	Broadband Topologies
<ul style="list-style-type: none">■ Inductive Load■ Resistive Feedback■ Cascode, Inductive Load, Inductive Degeneration	<ul style="list-style-type: none">■ Inductive Load■ Feedback■ Feedforward■ Cascode and Inductive Load	<ul style="list-style-type: none">■ Noise-Cancelling LNAs■ Reactance-Cancelling LNAs

Mainly Focus on this!


Resistor Input Matching

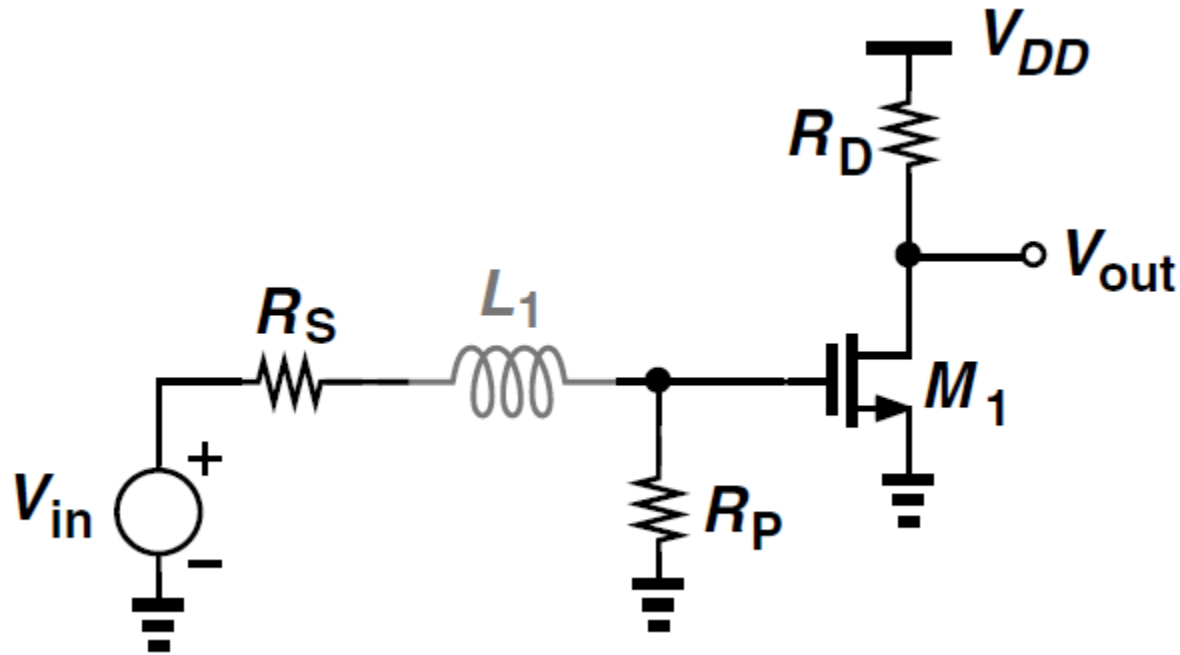

For $R_P \approx R_S$, the NF exceeds 3 dB—perhaps substantially.


Common Source with Inductive Load

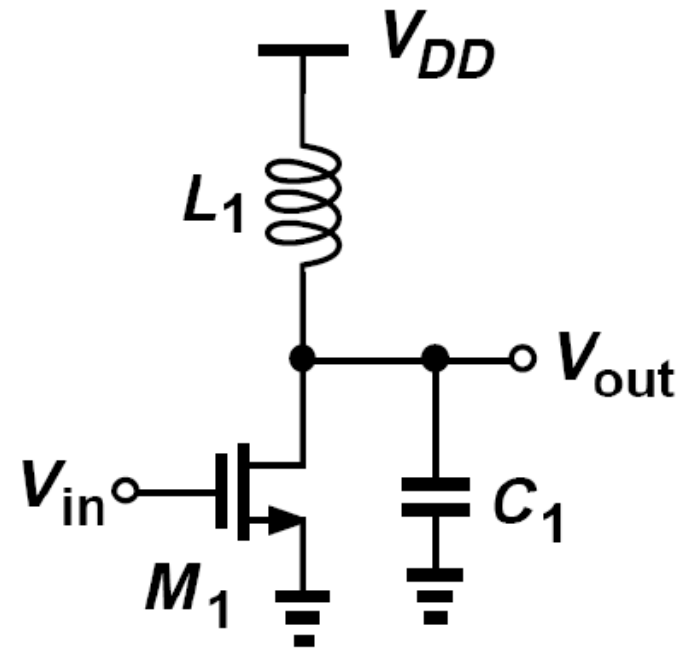- Can operate with very low supply voltages
- L_1 resonates with the total capacitance at the output node, affording a much higher operation frequency than does the resistively-loaded counterpart



How about the input matching?

Common Source with Inductive Load

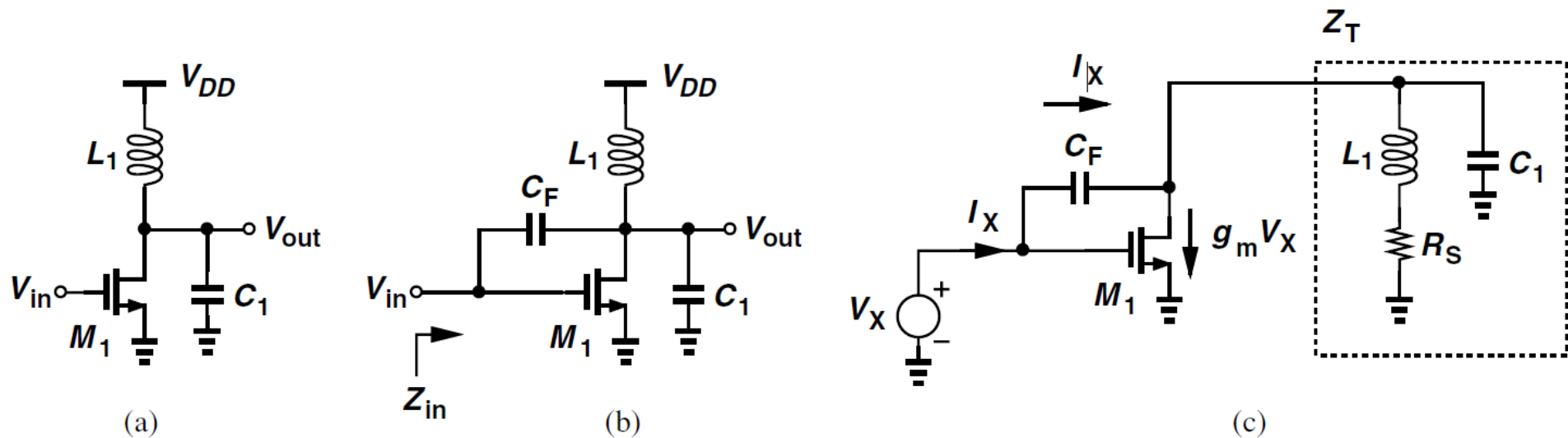

$$Z_{in}(s) = \frac{V_X}{I_X} = \frac{L_1(C_1 + C_F)s^2 + R_S(C_1 + C_F)s + 1}{[L_1C_1s^2 + (R_SC_1 + g_mL_1)s + 1 + g_mR_S]C_Fs}$$

While providing the possibility of $\text{Re}\{Z_{in}\} = 50 \, \Omega$ at the frequency of interest, the feedback capacitance C_F gives rise to a negative input resistance at other frequencies, potentially causing instability.