

---

# EE288 Data Conversions/Analog Mixed-Signal ICs

## Spring 2018

### Lecture 21: Pipelined ADC 3


Prof. Sang-Soo Lee  
[sang-soo.lee@sjsu.edu](mailto:sang-soo.lee@sjsu.edu)  
ENG-259

# Agenda


---

- Pipelined ADC Error Correction
  - Bit alignment
  - ADC Implementation Example
- OPAMP requirement
  - Gain
  - Bandwidth

# Pipelined ADC

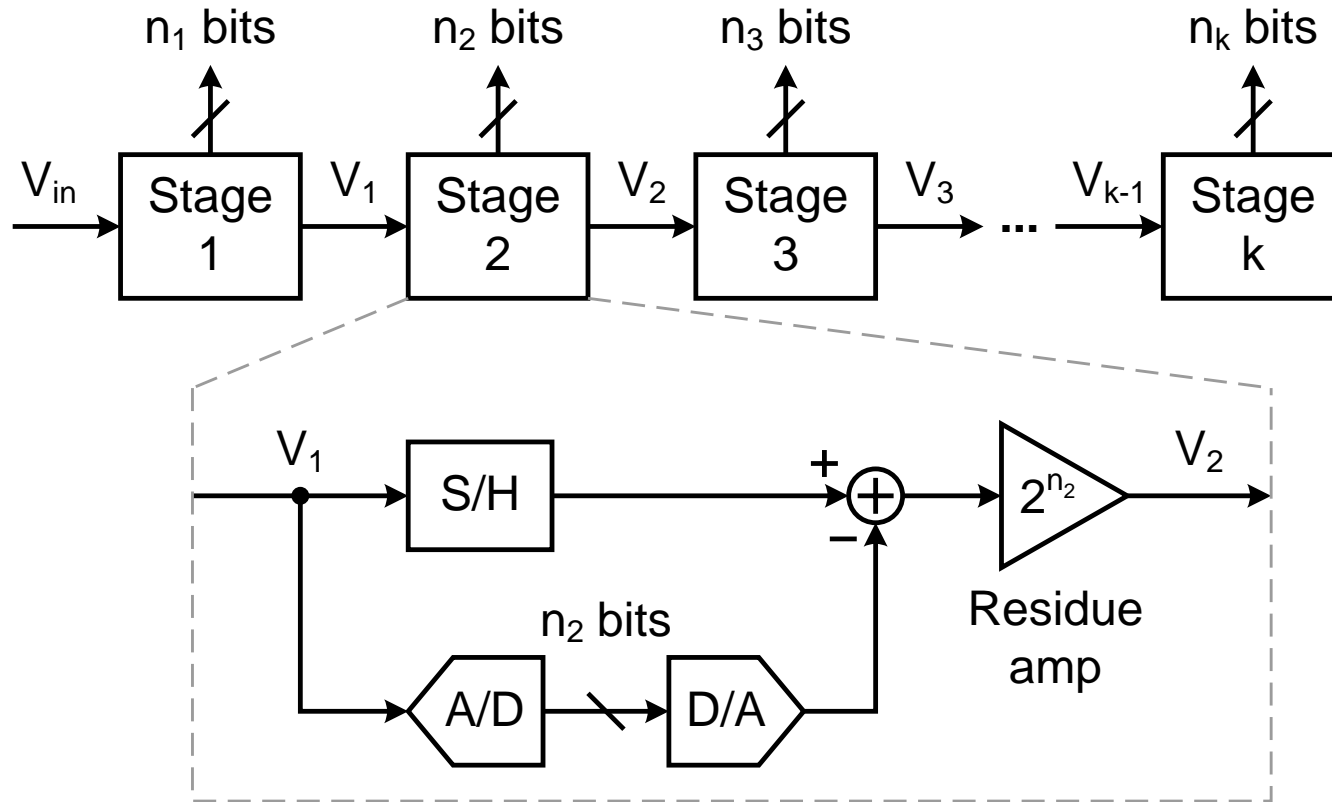


# Pipelining – Old Idea

 

U.S. DEPARTMENT OF THE INTERIOR, NATIONAL PARK SERVICE, EDISON NATIONAL HISTORIC SITE


# Pipelined ADC

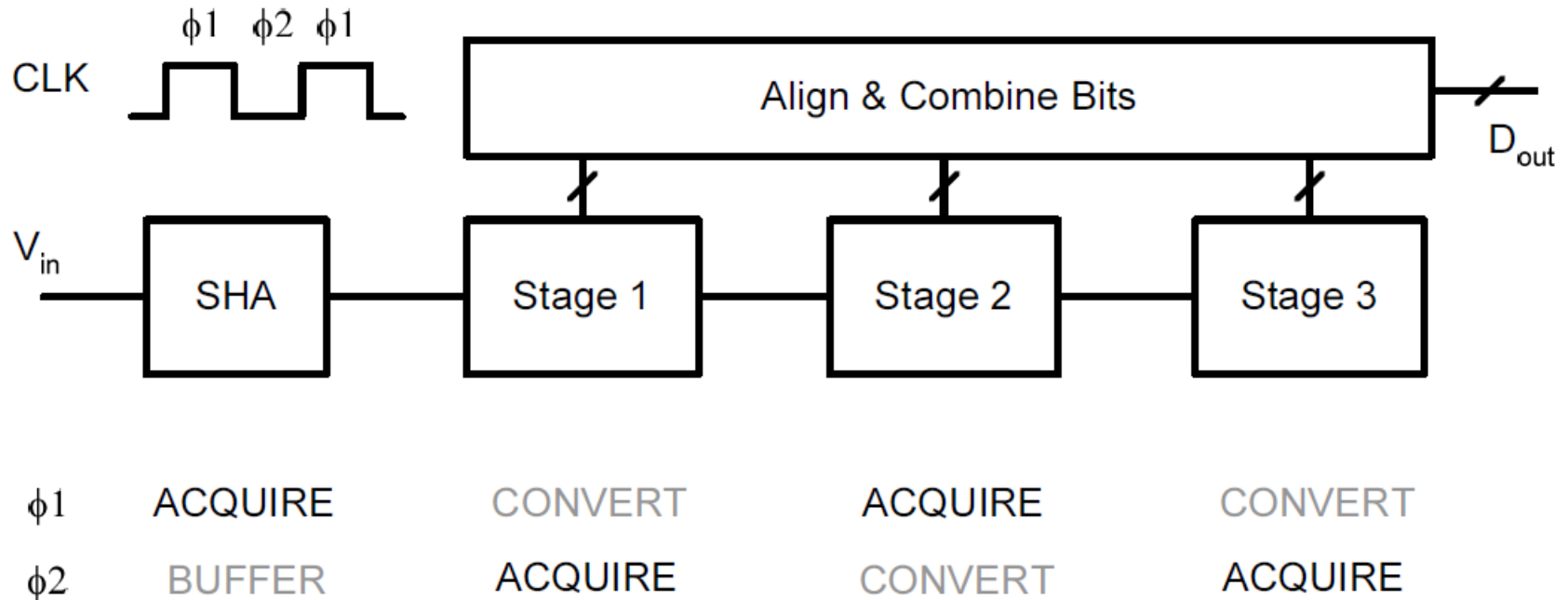

- Stages operate on the input signal like a shift register
- New output data every clock cycle, but each stage introduces  $\frac{1}{2}$  clock cycle latency

# Combining the Bits

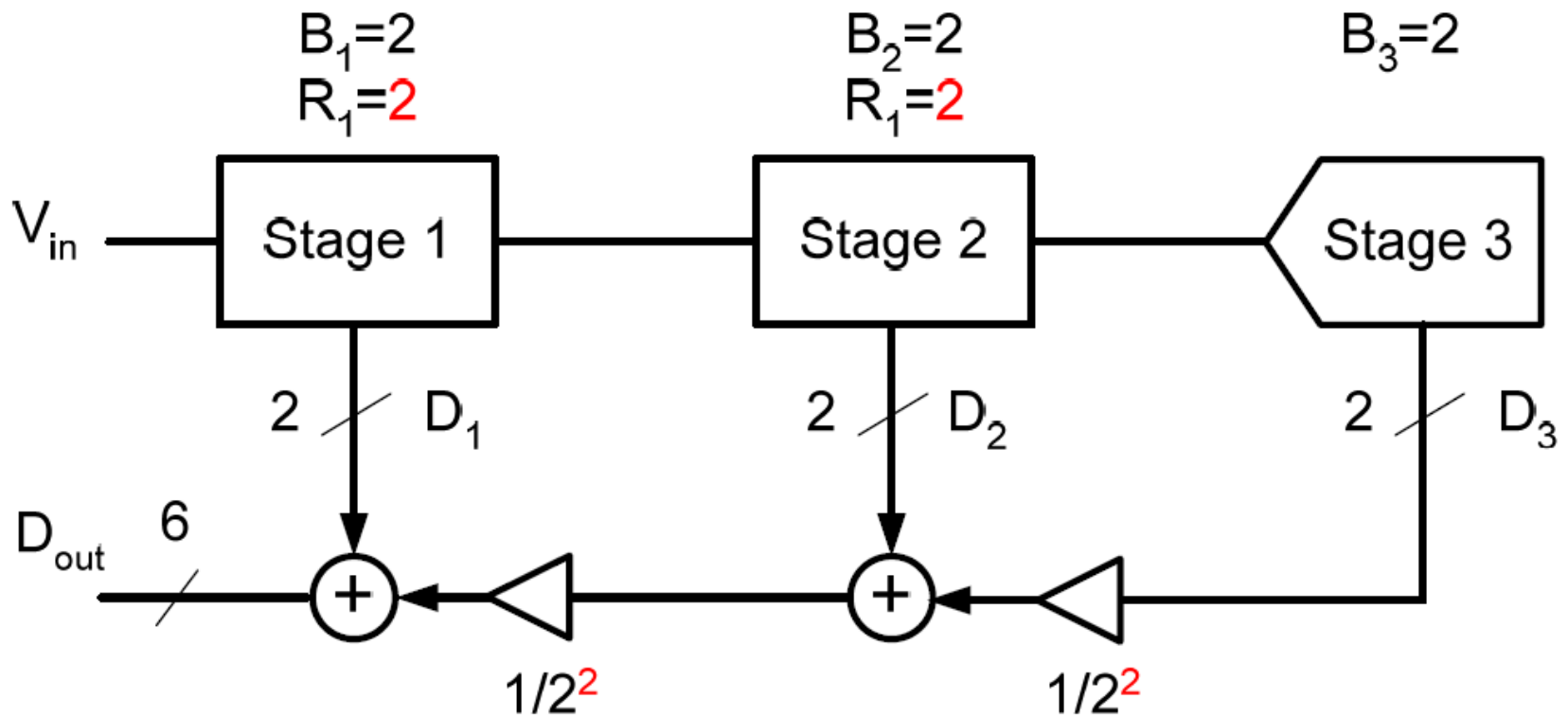- Example1: Three 2-bit stages, no redundancy




$$D_{out} = D_1 + \frac{1}{4}D_2 + \frac{1}{16}D_3$$
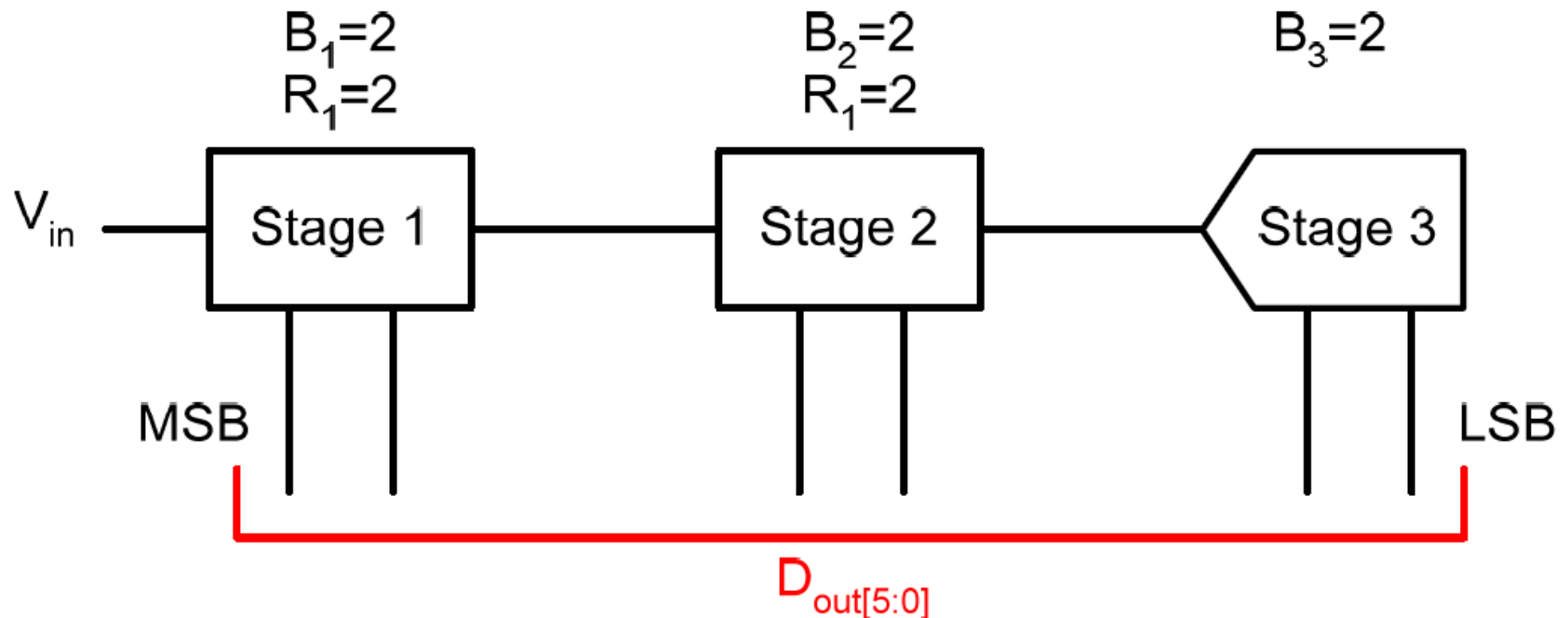
# Combining the Bits


$D_1$     **XX**  
 $D_2$         **XX**  
 $D_3$             **XX**  
-----  
 $D_{out}$     **DDDDDD**

- Only bit shifts
- No arithmetic circuits needed



# Combining the Bits

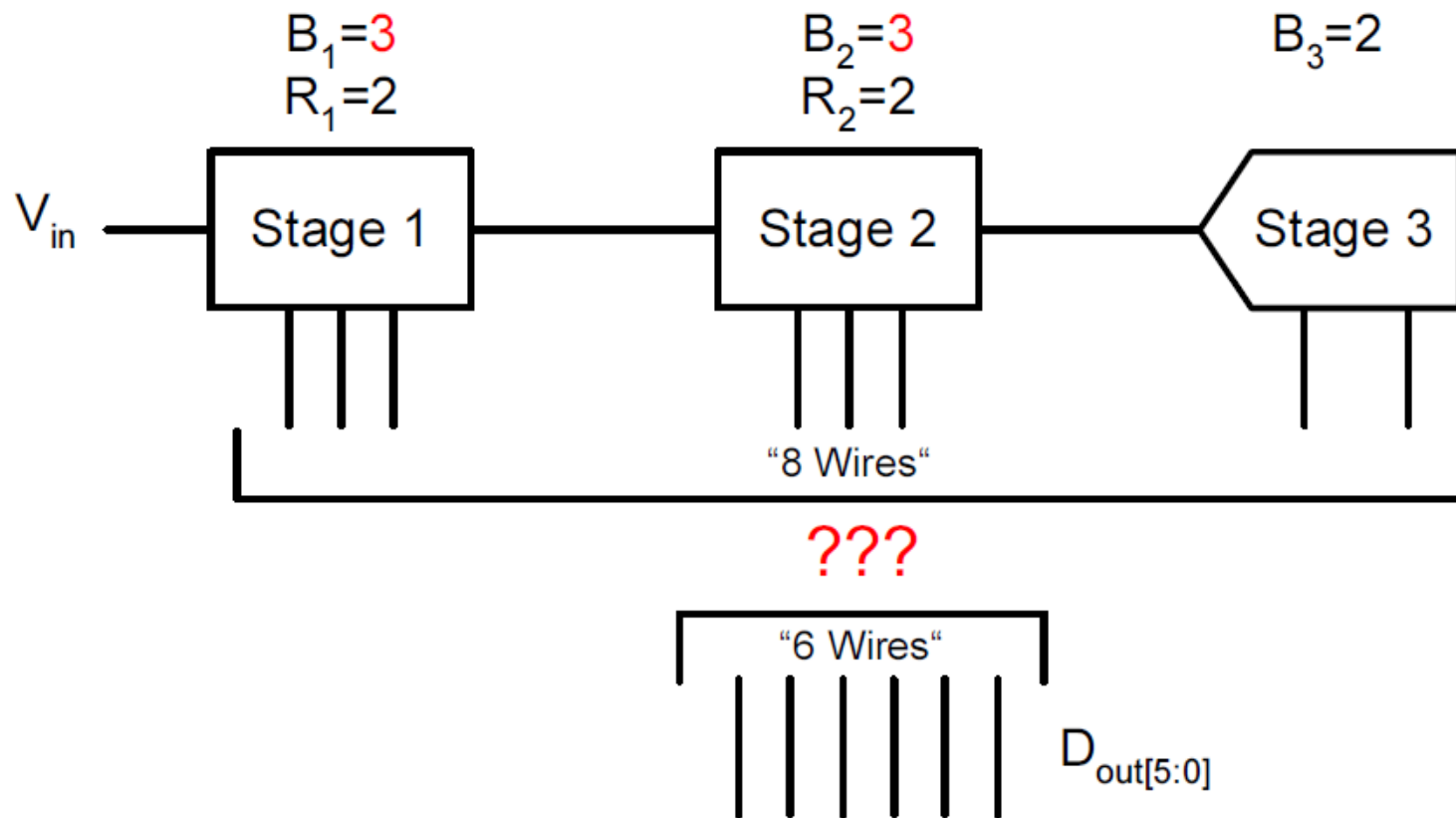- Example2: Three 2-bit stages, one bit redundancy in stages 1 and 2 (6-bit aggregate ADC resolution)






# Combining the Bits

$$D_{out} = D_1 + \frac{1}{4}D_2 + \frac{1}{16}D_3$$

D <sub>1</sub>	xxx
D <sub>2</sub>	xxx
D <sub>3</sub>	xx
-----	
D <sub>out</sub>	DDDDDD


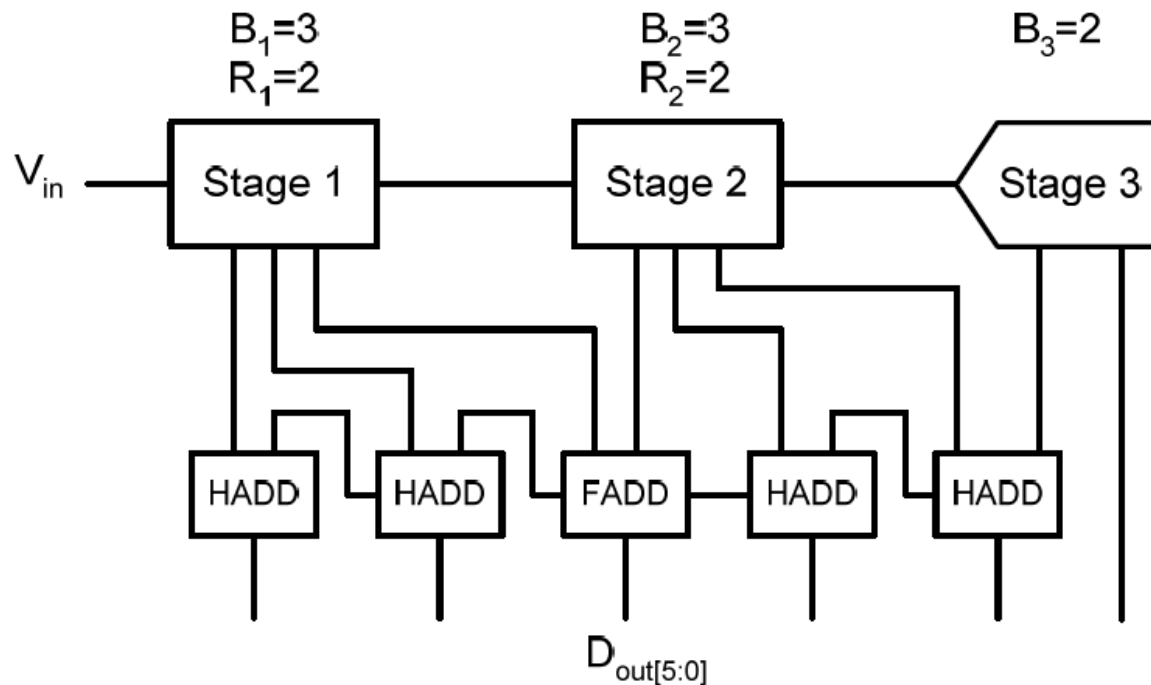
- Bits overlap
- Need adders (Still, no good reason for calling this "digital correction"...)




# 10-bit Pipelined ADC Implementation Example

## 8-Pipeline Stages

## 2b Flash ADC

 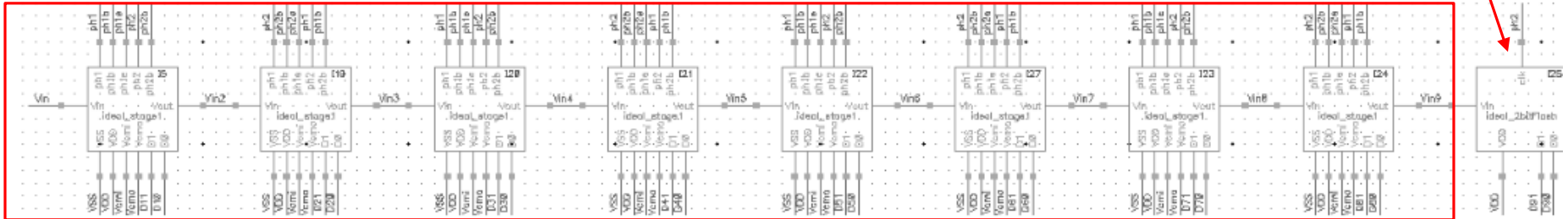


# Latches

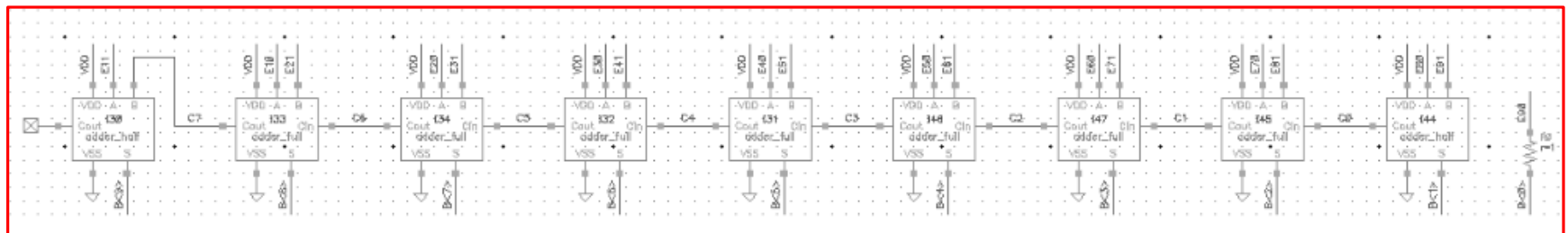

# Adders



# Stage Delay Structure Example

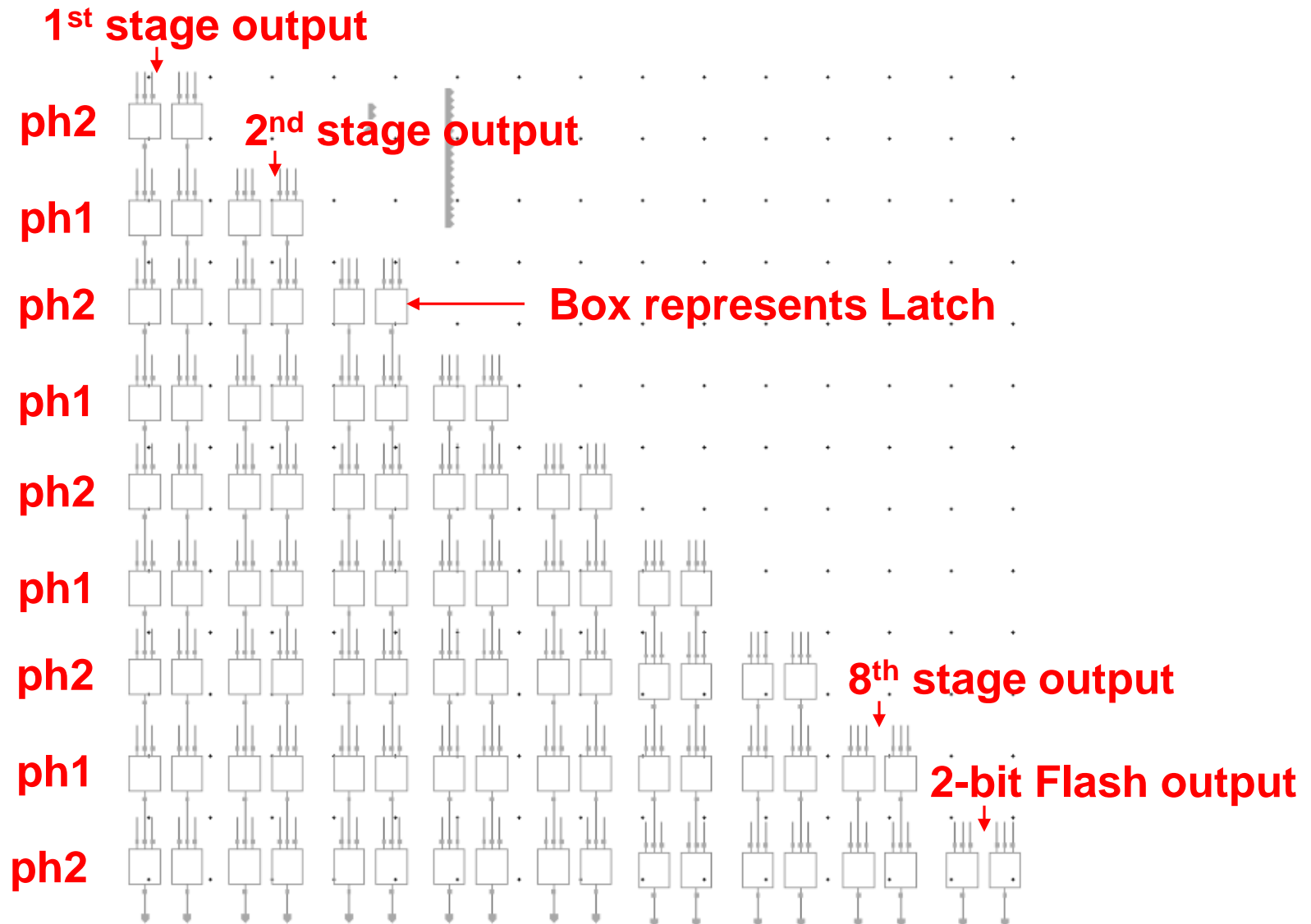

# No. of Comparators and Inter-stage Gain


- Number of Comparators for redundant stage design
  - $2^N - 2$
  - 2-bit  $\rightarrow 2^2 - 2 = 2$  Comparators
  - 3-bit  $\rightarrow 2^3 - 2 = 6$  Comparators
- Inter-stage MDAC gain requirement
  - $2^{N-1}$
  - 2-bit  $\rightarrow 2^{2-1} = 2$
  - 3-bit  $\rightarrow 2^{3-1} = 4$
- For MDAC gain of 4
  - $Q = C_1 \cdot V_1 = C_2 \cdot V_2$
  - Sample input signal into 4 capacitors during phase 1 :  $Q_1 = 4C \cdot V_{in}$
  - Flip-around to 1 capacitor during phase 1 :  $Q_2 = C \cdot V_{out}$
  - $Q_1 = Q_2 \rightarrow V_{out} = 4V_{in}$

# 1.5-bit/Stage Pipelined ADC

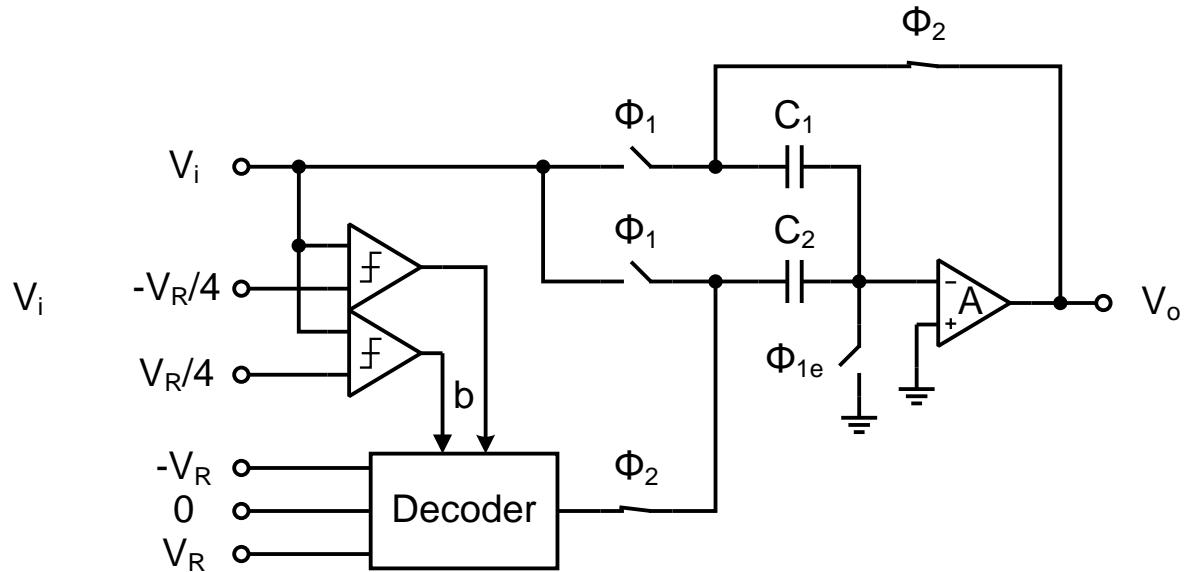 


- 2X gain + 3-level DAC + subtraction all integrated
- Digital redundancy relaxes the tolerance on CMP/RA offsets

## 2.5-bit/Stage Pipelined ADC

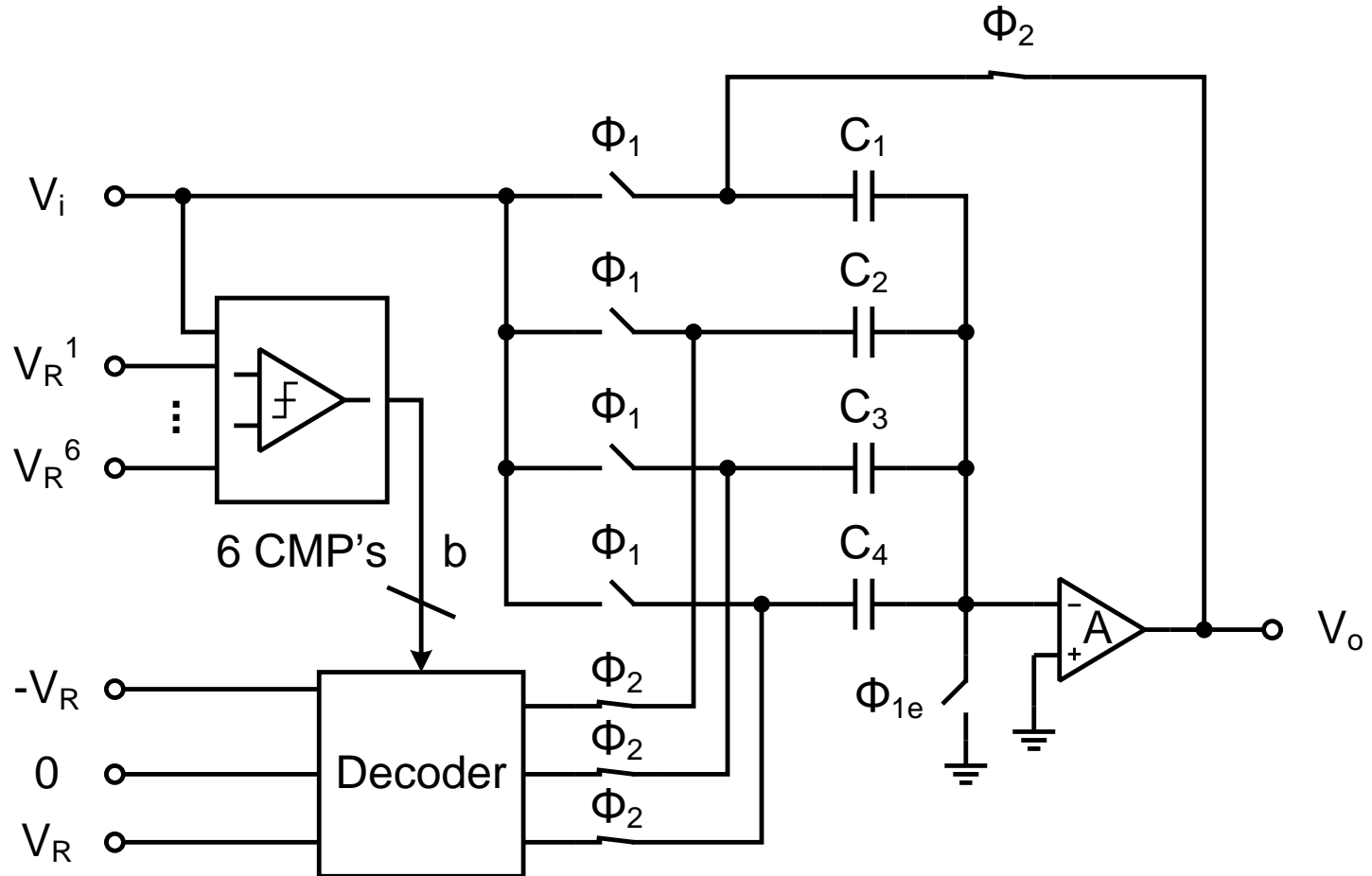

## 2.5-bit/Stage Pipelined ADC

 


- 6 comparators + 7-level DAC are required
- Max tolerance on comparator offset is  $\pm V_R/8$

# Example 14-bit Pipelined ADC

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 36, NO. 12, DECEMBER 2001

A 3-V 340-mW 14-b 75-Msample/s CMOS ADC With 85-dB SFDR at Nyquist Input

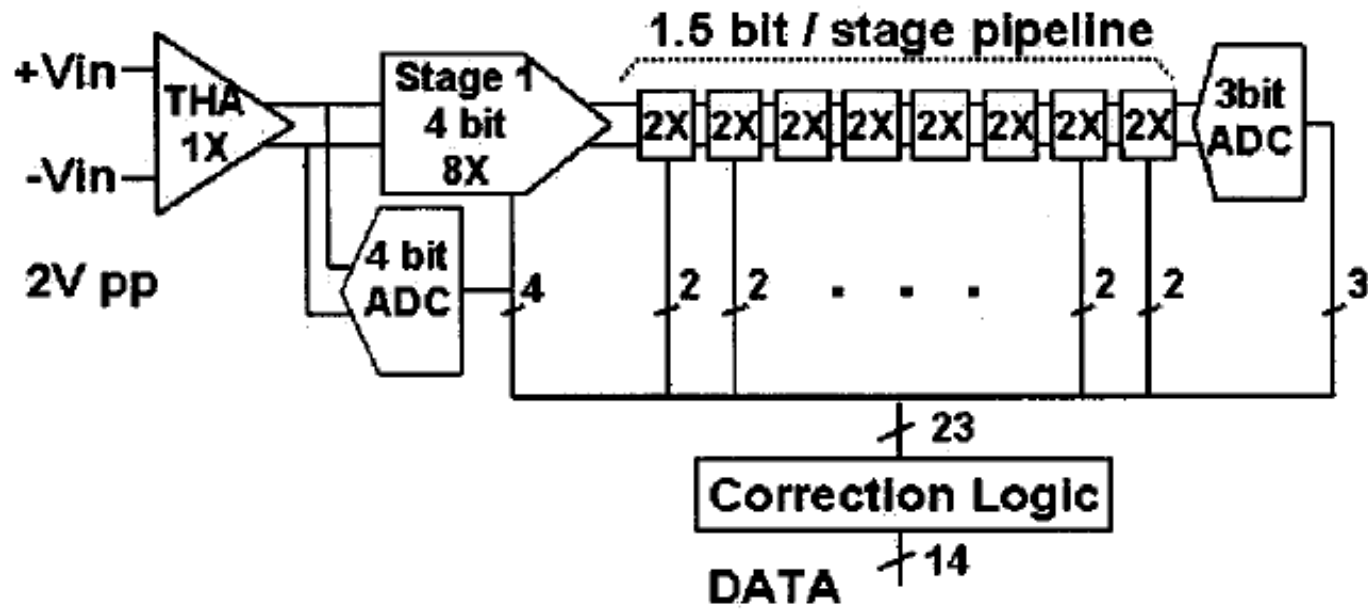
Wenhua (Will) Yang, *Member, IEEE*, Dan Kelly, *Member, IEEE*, Iuri Mehr, *Member, IEEE*, Mark T. Sayuk, *Member, IEEE*, and Larry Singer, *Member, IEEE*






# 14-bit Pipelined ADC

## Charge-redistribution THA

 


# 14-bit Pipelined ADC

## Flip-around THA

 


# 14-bit Pipelined ADC

## Amplifier in Flip-around THA

 

# 14-bit Pipelined ADC

## Amplifier in Stage 1

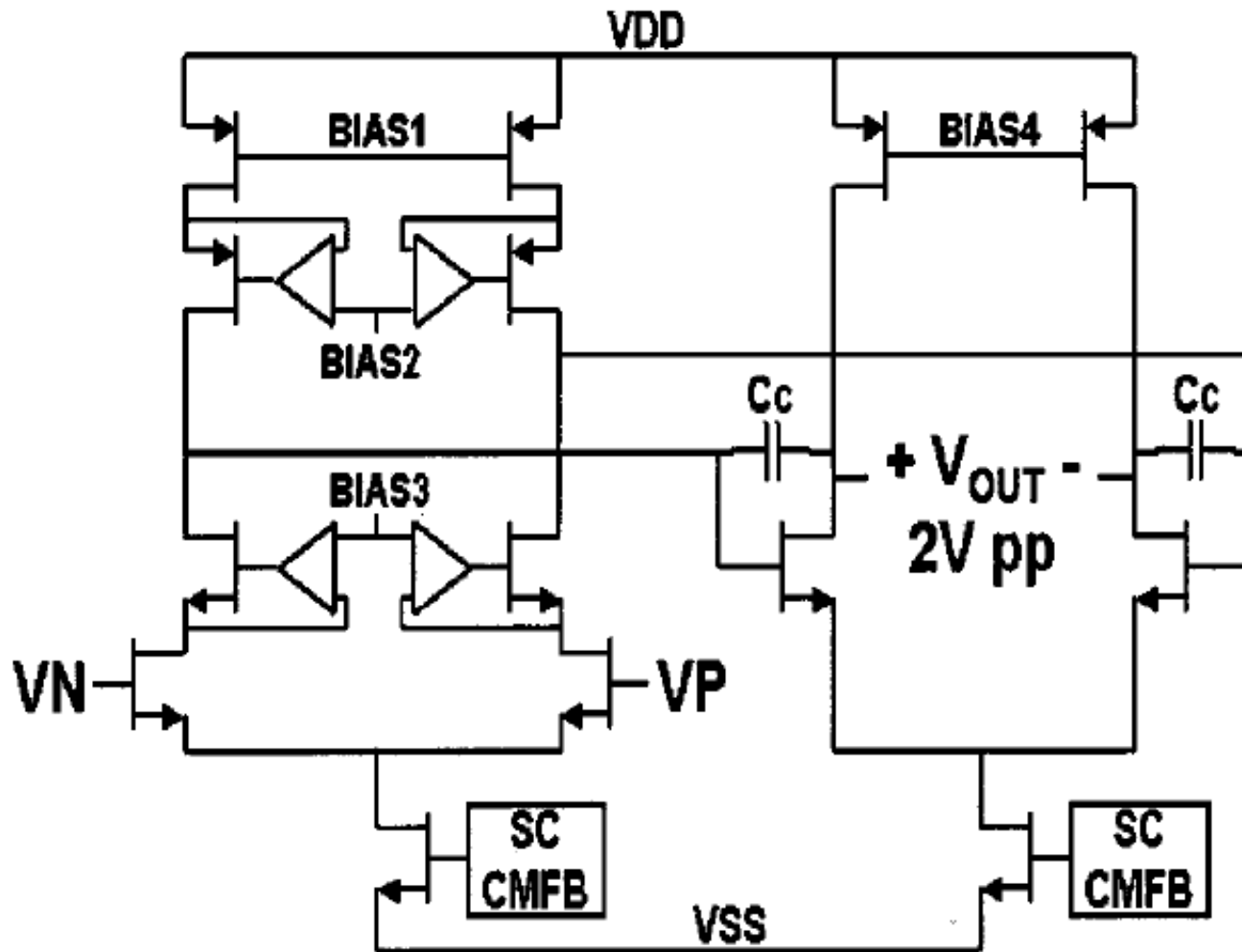

# OPAMP Gain Requirement for N-bit ADC

OPAMP is always used in closed loop configuration.

OPAMP Closed-loop Response: 
$$V_{\text{out}} = G \times V_{\text{in}} \left( \frac{1}{1 + \frac{1}{A \times \beta}} \right) \left( 1 - e^{-\frac{t}{\tau}} \right)$$

Assume Gain Error should be less than ¼ LSB

$$\frac{1}{\beta A} < \frac{1}{4} \text{ LSB} \rightarrow \frac{1}{\beta A} < \frac{1}{4} \frac{V_{FS}}{2^N}$$

$$A > \frac{4 \cdot 2^N}{\beta \cdot V_{FS}}$$

Resolution	Full Scale	Beta	Gain (dB)	Gain (dB)
N	V <sub>FS</sub> (Volt)	β	$4 \cdot 2^N / (\beta \cdot V_{FS})$	20log(x)
10	1	1	4096	72
10	1	0.5	8192	78
11	1	1	8192	78
11	1	0.5	16384	84
12	1	1	16384	84
12	1	0.5	32768	90
13	1	1	32768	90
13	1	0.5	65536	96
14	1	1	65536	96
14	1	0.5	131072	102

# OPAMP Bandwidth Requirement for N-bit ADC

Assume Settling Error should be less than 1/2 LSB

$$e^{-t/\tau} < \frac{1}{2} \text{ LSB} \rightarrow e^{-t/\tau} < \frac{1}{2} \frac{V_{FS}}{2^N} \rightarrow \frac{t}{\tau} > (N + 1)\ln(2) - \ln(V_{FS})$$

$$t = \frac{T_s}{2} = \frac{1}{2f_s}$$

$$\tau = \frac{1}{\omega_{-3dB}} = \frac{1}{2\pi f_{-3dB}} = \frac{1}{2\pi \beta f_u}$$

$$\frac{t}{\tau} = \frac{1}{2f_s} 2\pi \beta f_u > (N + 1)\ln(2) - \ln(V_{FS})$$

$$f_u > \frac{f_s}{\pi\beta} [(N + 1)\ln(2) - \ln(V_{FS})]$$

$$\ln(2) = 0.693$$

Resolution	Full Scale	Beta	Sampling Rate	UGB	UGB(MHz)	fu/fs
N	V <sub>FS</sub> (Volt)	β	fs	fu	fu	fu = k fs
10	1	1	1.00E+08	2.43E+08	243 MHz	fu = 2.5 fs
10	1	0.5	1.00E+08	4.85E+08	485 MHz	fu = 5 fs
11	1	1	1.00E+08	2.65E+08	265 MHz	
11	1	0.5	1.00E+08	5.30E+08	530 MHz	
12	1	1	1.00E+08	2.87E+08	287 MHz	fu = 3 fs
12	1	0.5	1.00E+08	5.74E+08	574 MHz	fu = 6 fs
13	1	1	1.00E+08	3.09E+08	309 MHz	
13	1	0.5	1.00E+08	6.18E+08	618 MHz	
14	1	1	1.00E+08	3.31E+08	331 MHz	fu = 3.3 fs
14	1	0.5	1.00E+08	6.62E+08	662 MHz	fu = 6.6 fs