

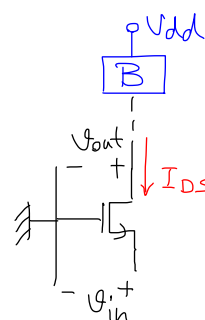
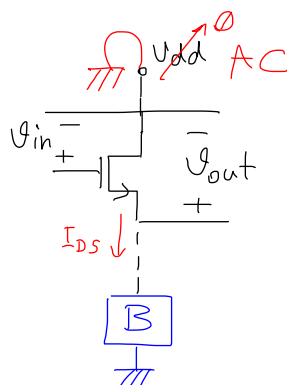
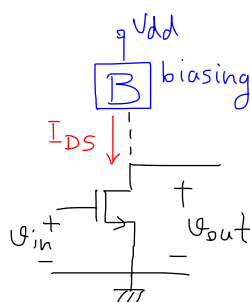
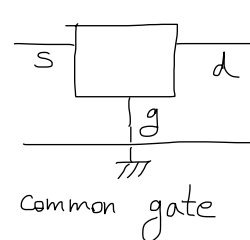
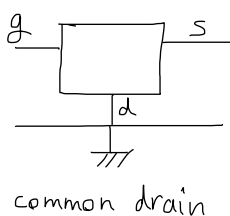
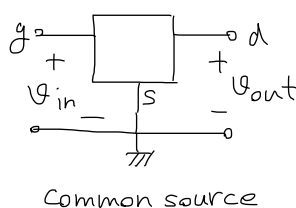
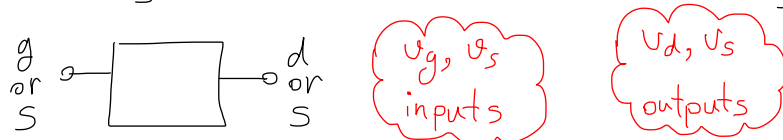
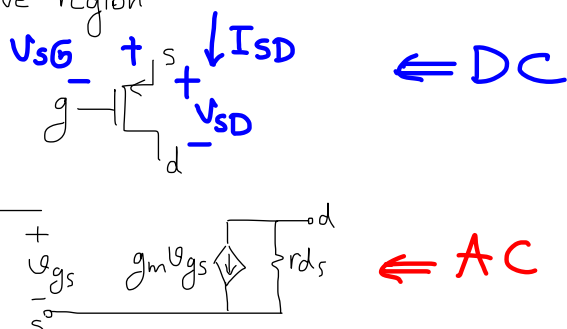


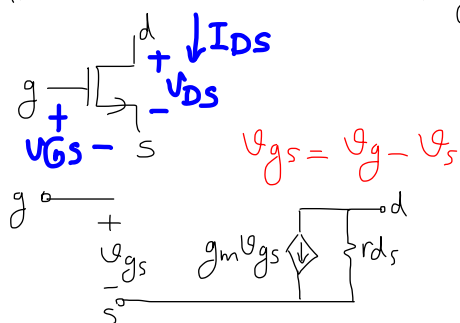* Assume that transistors always operate in active region




* How to build bias network?


Example for Common Source



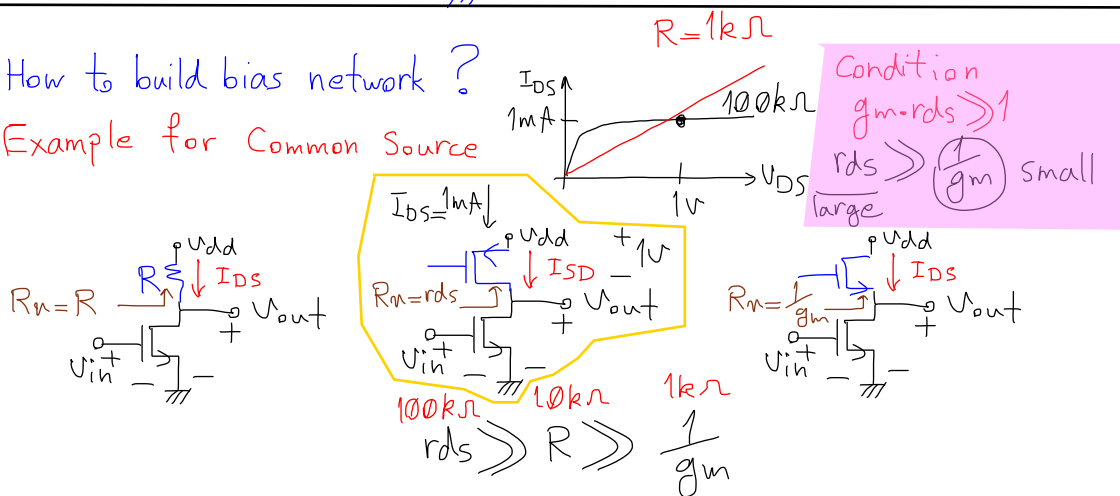


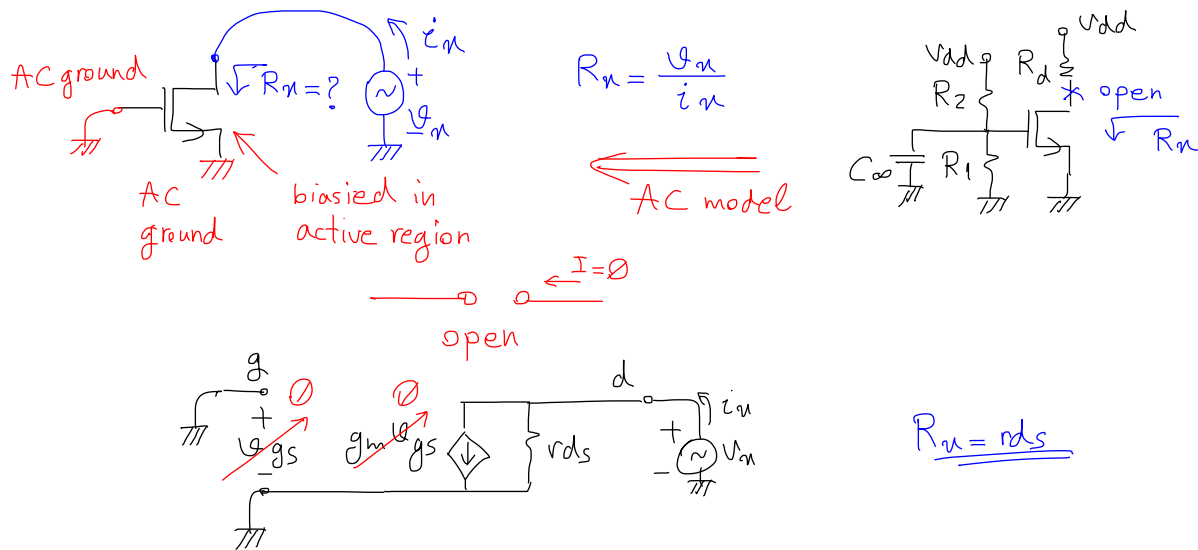* Question: What is resistance seen at drain?



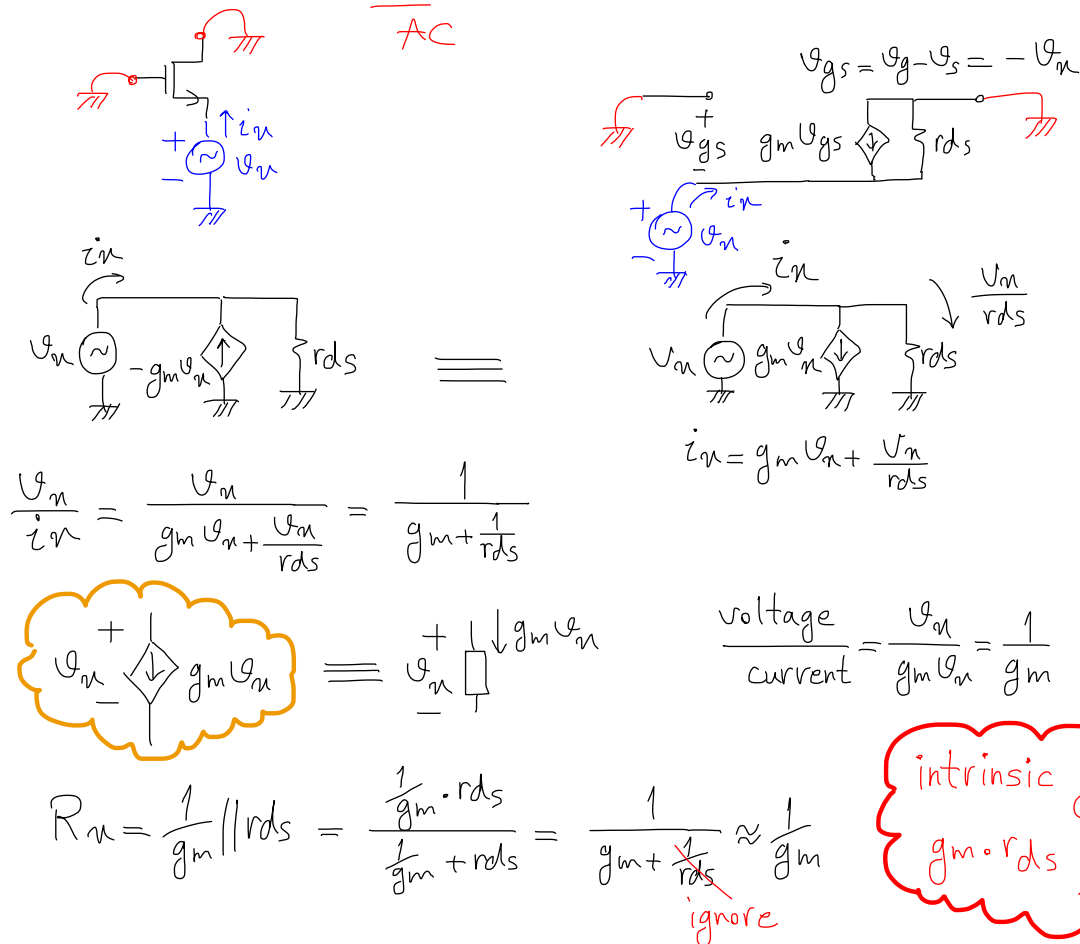
* Question: What is resistance seen @ source?



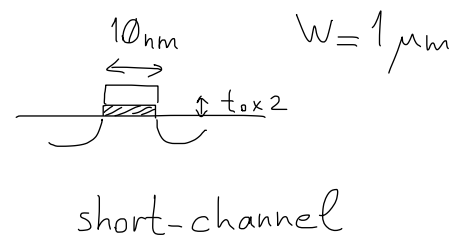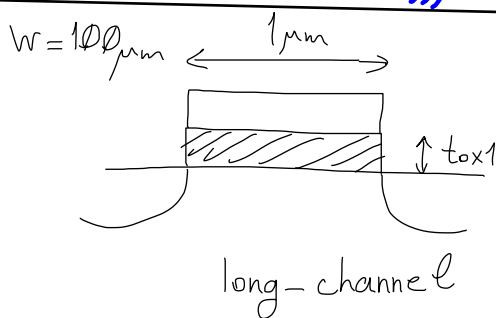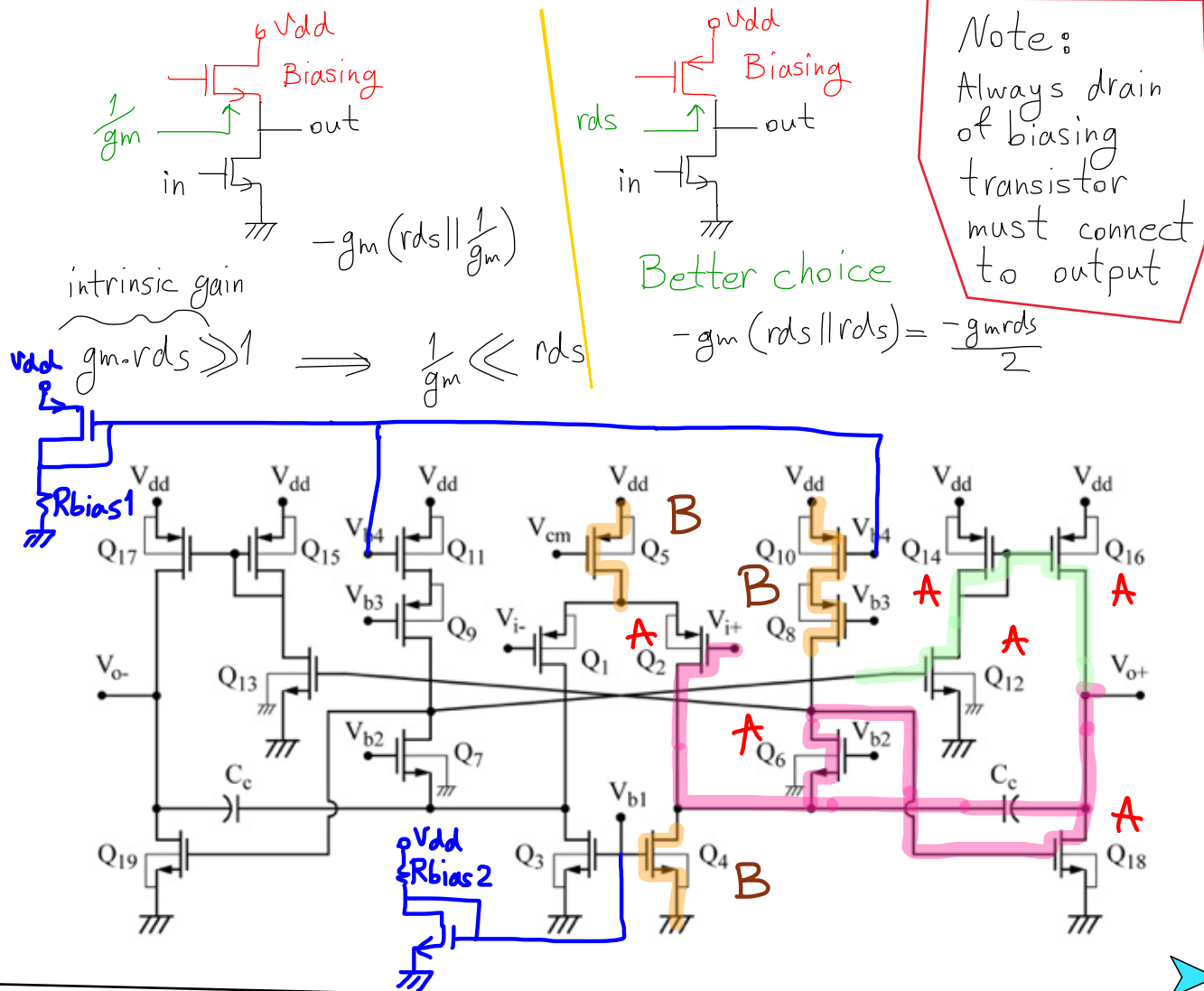




$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})$$
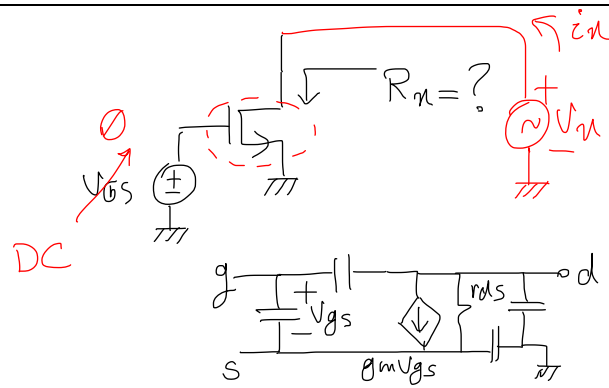
$$C_{ox} = \frac{\epsilon_0 \epsilon_r}{t_{ox}}$$






- * finding resistance at a node
 1. connect a V_n test source to that node
 2. create AC model
 3. find $R_n = \frac{V_n}{i_n}$

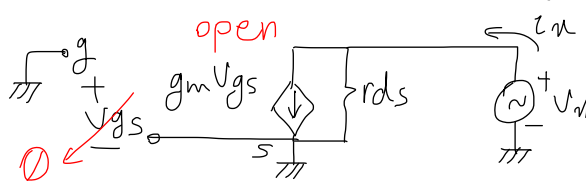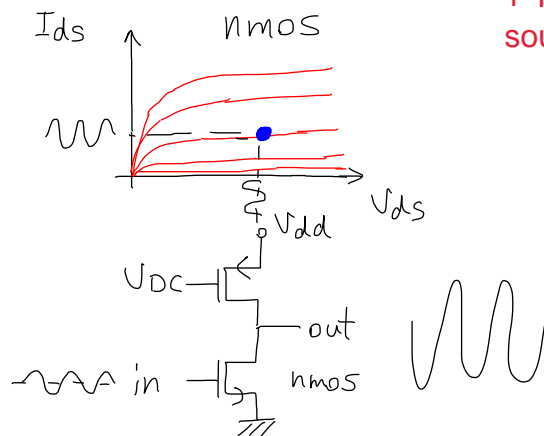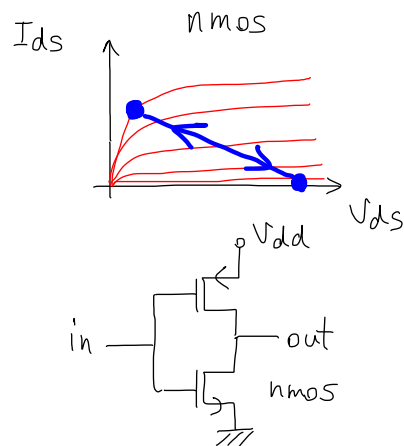- + Turn off any other independent source



$$R_n = \frac{V_n}{i_n} = r d_s$$

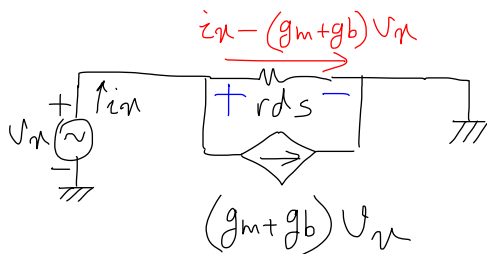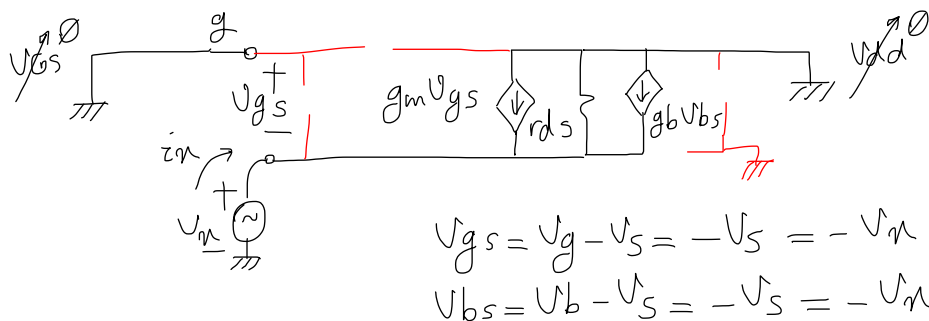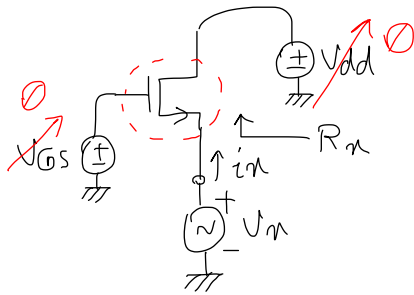->> How to get the resistance from the source terminal (while including Body Effect) ?




$$V_n = r_{ds} [i_n - (g_m + g_b) V_n]$$

$$R_n = \frac{V_n}{i_n} = \frac{r_{ds}}{1 + (g_m + g_b) r_{ds}} = \frac{1}{g_m + g_b}$$

ignore

$g_m \gg g_b$
 $g_m \cdot r_{ds} \gg 1$

$$R_n \approx \frac{1}{g_m}$$



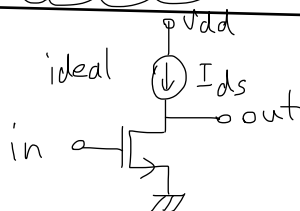


current source resistance

$$-g_m(r_{ds} \parallel \infty) \approx -g_m r_{ds}$$

this is the maximum gain of a single transistors

->> The Nanowire SGFET Technology

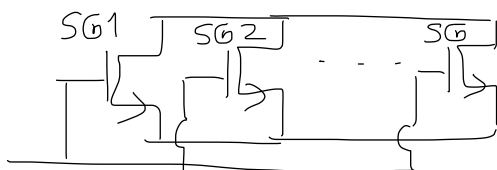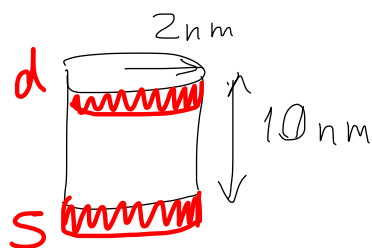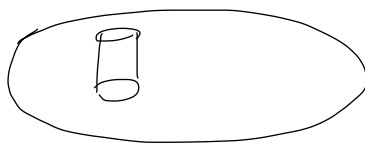

← Transistors have to be connected like this to increase the W in this technology ..
(We can't just modify the L or W of an individual transistor in this technology)