

---

# EE223 Analog Integrated Circuits

## Fall 2018

### Homework #5 Hint


Sang-Soo Lee  
Electrical Engineering Department  
San Jose State University  
[sang-soo.lee@sjsu.edu](mailto:sang-soo.lee@sjsu.edu)

# 2-Stage OPAMP with RC compensation


Technology: 0.18um CMOS, VDD=1.8V, Lmin = 180nm

Target Spec:

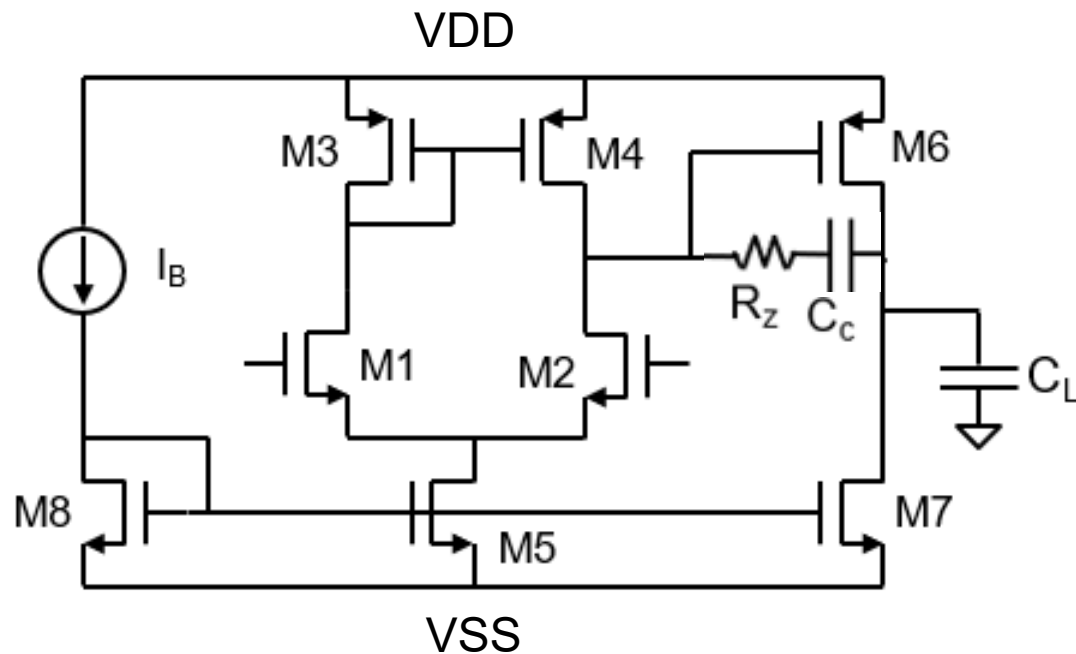- DC gain = 60dB
- GBW = 100MHz
- PM = 60°
- Cload = 5pF



# Small-Signal Model of the OPAMP

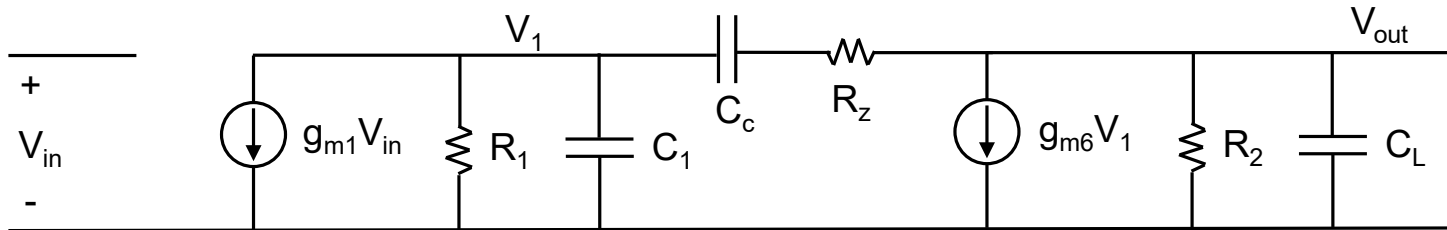

$$A_v = A_{v1} A_{v2} = -g_{m1}R_1g_{m6}R_2$$

$$p1 \approx -1/(R_1g_{m6}R_2C_c)$$

$$p2 \approx -g_{m6}/C_L \quad \text{assuming } C_L \text{ is very large compared to } C_1 \text{ and } C_c$$

$$z = 1 / [(1/ g_{m6} - R_z)C_c]$$

$$GBW = A_v \times p1 = g_{m1}/C_c$$

$$R_z = \frac{1}{g_{m6}} \left( 1 + \frac{C_L}{C_c} \right) \text{ to cancel } p2 \text{ with } z$$

# Design Information

---

## Design Spec

- $A_v = 60 \text{ dB}$
- $\text{GBW} = 100 \text{ MHz}$
- $\text{PM} = 60^\circ$
- $C_L = 5 \text{ pF}$

## Assumption for Hand Calculation

- $KP_n = \mu_n C_{ox} = 300 \text{ uA/V}^2$
- $KP_p = \mu_p C_{ox} = 160 \text{ uA/V}^2$
- $V_{dsat} = 0.2 \text{ V}$
- $I_B = 100 \text{ uA}$

# Design Procedure

1.  $GBW = g_{m1} / C_c = \omega_u$

- Pick  $C_c = C_L / 3$
- $g_{m1} = 2\pi f_u \cdot C_c$

2. If Slew-Rate Spec is given

- $SR = 2I_1 / C_c \rightarrow I_1 = SR \cdot C_c / 2$
- $g_{m1} = \sqrt{2KP \cdot \left(\frac{W}{L}\right)_1 \cdot I_1} \rightarrow \left(\frac{W}{L}\right)_1 = \frac{g_{m1}^2}{2KP \cdot I_1}$

3. If Slew-Rate Spec is not given

- Pick  $V_{dsat1} = 0.2V \rightarrow I_1 = \frac{g_{m1} \cdot V_{dsat1}}{2}$
- $I_D = \frac{KP}{2} \frac{W}{L} (V_{gs} - V_t)^2 \rightarrow \left(\frac{W}{L}\right)_1 = \frac{2 \cdot I_1}{KP \cdot V_{dsat1}^2}$

4. If ICMR (Input Common Mode Range) Spec is given

- Choose M3 size based on  $ICMR_{max}$  requirement  $\rightarrow$  See next page
- Choose M5 size based on  $ICMR_{min}$  requirement  $\rightarrow$  See next page


5. If ICMR (Input Common Mode Range) Spec is not given

- Pick  $V_{dsat3} = 0.2V \rightarrow \left(\frac{W}{L}\right)_3 = \frac{2 \cdot I_3}{KP \cdot V_{dsat3}^2}$
- Pick  $V_{dsat5} = 0.2V \rightarrow \left(\frac{W}{L}\right)_5 = \frac{2 \cdot I_5}{KP \cdot V_{dsat5}^2}$


6. Choose  $g_{m6} = 10 g_{m1}$  for 60° PM  $\rightarrow I_6 = 10 I_1$  if  $V_{dsat6} = V_{dsat1} = 200mV$  since  $g_m = \frac{2 \cdot I}{V_{dsat}}$

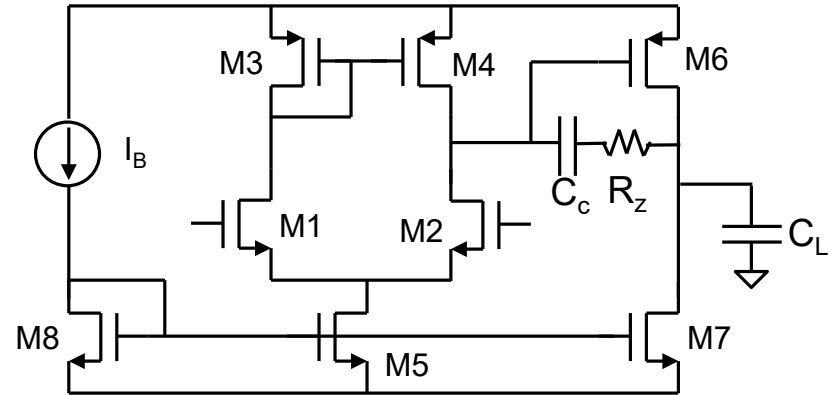7. Calculate  $I_6 = \frac{g_{m6} \cdot V_{dsat6}}{2} \rightarrow \left(\frac{W}{L}\right)_6 = \frac{2 \cdot I_6}{KP \cdot V_{dsat6}^2}$

[ $V_{dsat6}$  is based on OCMR requirement]



# W/L Calculation from CMR Requirement

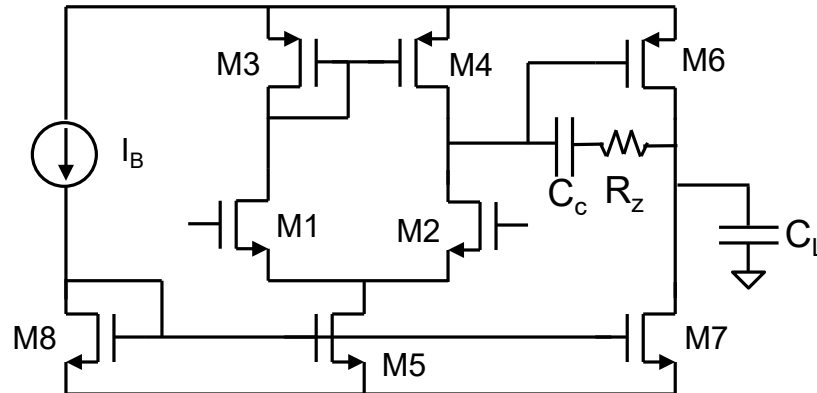
$$\text{ICMR}_{\max}$$

- $ICMR_{\max} - V_{gs1} + V_{dsat1} = V_{DD} - V_{sg3}$
- $ICMR_{\max} - V_{th1} = V_{DD} - (V_{th3} + V_{dsat3})$
- $ICMR_{\max} \approx V_{DD} - V_{dsat3}$  assuming  $V_{th1} = V_{th3}$
- $V_{dsat3} = V_{DD} - ICMR_{\max}$
- $I_D = \frac{KP}{2} \frac{W}{L} (V_{gs} - V_t)^2 \rightarrow \left(\frac{W}{L}\right)_3 = \frac{2 \cdot I_{D3}}{KP \cdot V_{dsat3}^2}$

$$\text{ICMR}_{\min}$$

- $ICMR_{min} - V_{gs1} = V_{dsat5}$
- $V_{dsat5} = ICMR_{min} - (V_{th1} + V_{dsat1})$
- Use  $V_{th1}$  from simulation and choose  $V_{dsat1} = 200mV$
- $\left(\frac{W}{L}\right)_5 = \frac{2 \cdot I_{D5}}{K_P \cdot V_{dsat5}^2}$

# Homework#5 Design Spec

## Target Design Spec

- $A_v = 60 \text{ dB}$
- $\text{GBW} = 100 \text{ MHz}$
- $\text{PM} = 60^\circ$
- $C_L = 5 \text{ pF}$

## Assumption for Hand Calculation

- $KP_n = \mu_n C_{ox} = 300 \text{ uA/V}^2$
- $KP_p = \mu_p C_{ox} = 160 \text{ uA/V}^2$
- $V_{dsat} = 0.2 \text{ V}$
- $I_B = 100 \text{ uA}$
- Cancel p2 with z  $\rightarrow R_z = \frac{1}{g_{m6}} \left( 1 + \frac{C_L}{C_c} \right)$

# Example Calculation

$$f_u = \frac{1}{2\pi} \frac{g_{m1}}{C_c} = 100\text{MHz}$$

$$C_L = 5 \text{ pF}$$

$$C_c = C_L / 3 = 1.67 \text{ pF}$$

$$g_{m1} = 2\pi \cdot 100\text{MHz} \cdot C_c = 2\pi \cdot 100\text{MHz} \cdot 1.67\text{pF} = 2\pi \cdot 100\text{MHz} \cdot 1.67\text{pF} = 1.05\text{mS}$$


$$I_1 = \frac{g_{m1} \cdot V_{dsat1}}{2} = \frac{1.05\text{m} \cdot 0.2}{2} = 105 \text{ uA} \rightarrow \text{Choose } I_1 = 100 \text{ uA in simulation}$$

$$I_1 = I_2 = I_3 = I_4 = 100 \text{ uA}$$

$$\left(\frac{W}{L}\right)_1 = \frac{2 \cdot I_1}{K_P \cdot V_{dsat1}^2} = \frac{2 \cdot 100\text{u}}{300\text{u} \cdot 0.2^2} = 16.67 \rightarrow \text{Choose } \left(\frac{W}{L}\right)_1 = 18 = 2\left(\frac{9}{1}\right)$$


$$\left(\frac{W}{L}\right)_3 = \frac{2 \cdot I_3}{K_P \cdot V_{dsat3}^2} = \frac{2 \cdot 100\text{u}}{160\text{u} \cdot 0.2^2} = 31.25 \rightarrow \text{Choose } \left(\frac{W}{L}\right)_3 = 4\left(\frac{9}{1}\right)$$
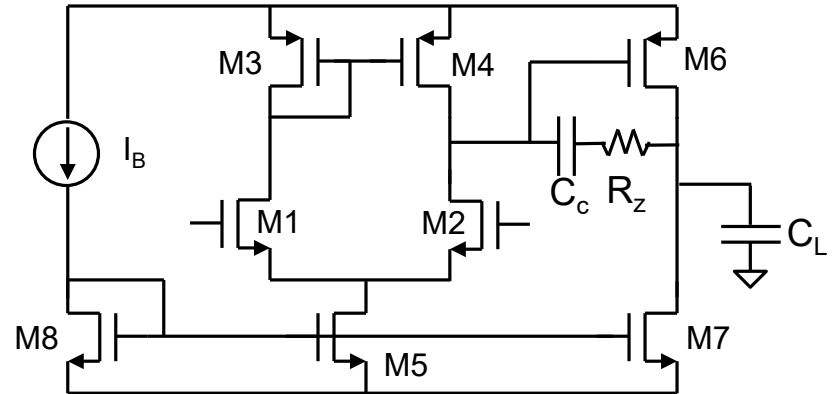
$$\left(\frac{W}{L}\right)_5 = \frac{2 \cdot I_5}{K_P \cdot V_{dsat5}^2} = \frac{2 \cdot 200\text{u}}{300\text{u} \cdot 0.2^2} = 33.35 \rightarrow \text{Choose } \left(\frac{W}{L}\right)_5 = 4\left(\frac{9}{1}\right)$$





# Example Calculation - Continued

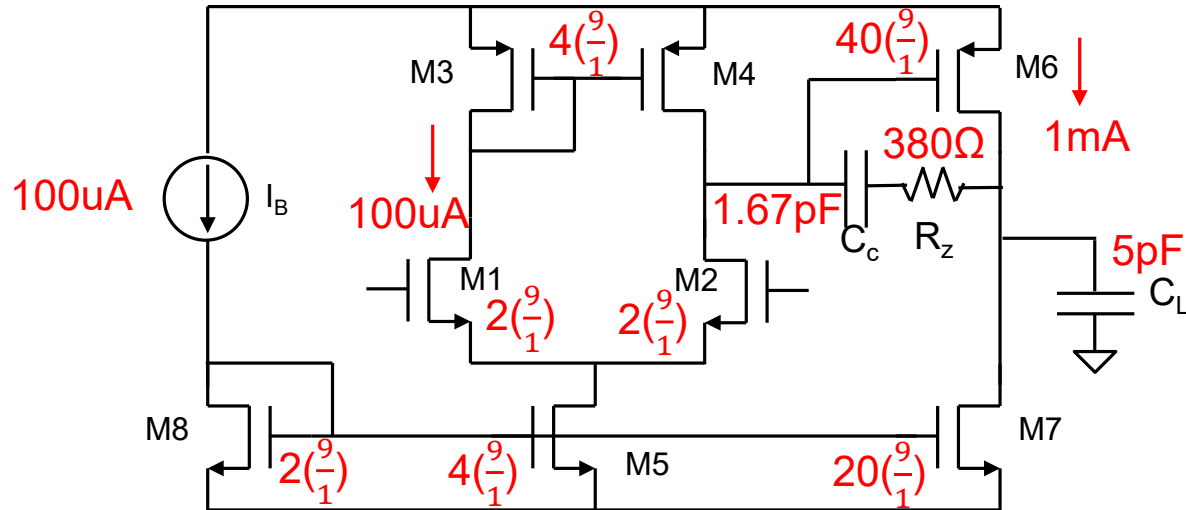

Choose  $g_{m6} = 10 g_{m1}$  for 60° PM

$$g_{m6} = 10 g_{m1} = 10.5 \text{ mS}$$

$$I_6 = \frac{g_{m6} \cdot V_{dsat6}}{2} = \frac{10.5 \text{ m} \cdot 0.2}{2} = 1.05 \text{ mA} \rightarrow \text{Choose } I_6 = 1 \text{ mA in simulation}$$


$$I_6 = I_7 = 1 \text{ mA}$$

$$\left(\frac{W}{L}\right)_6 = 10 \cdot \left(\frac{W}{L}\right)_4 = 10 \cdot 4\left(\frac{9}{1}\right) \rightarrow \text{Choose } \left(\frac{W}{L}\right)_6 = 40\left(\frac{9}{1}\right)$$


$$\left(\frac{W}{L}\right)_7 = 5 \cdot \left(\frac{W}{L}\right)_5 = 5 \cdot 4\left(\frac{9}{1}\right) \rightarrow \text{Choose } \left(\frac{W}{L}\right)_7 = 20\left(\frac{9}{1}\right)$$

$$R_Z = \frac{1}{10.5 \text{ m}} \left(1 + \frac{5}{1.67}\right) = 380 \Omega$$


# 2-Stage OPAMP Schematic

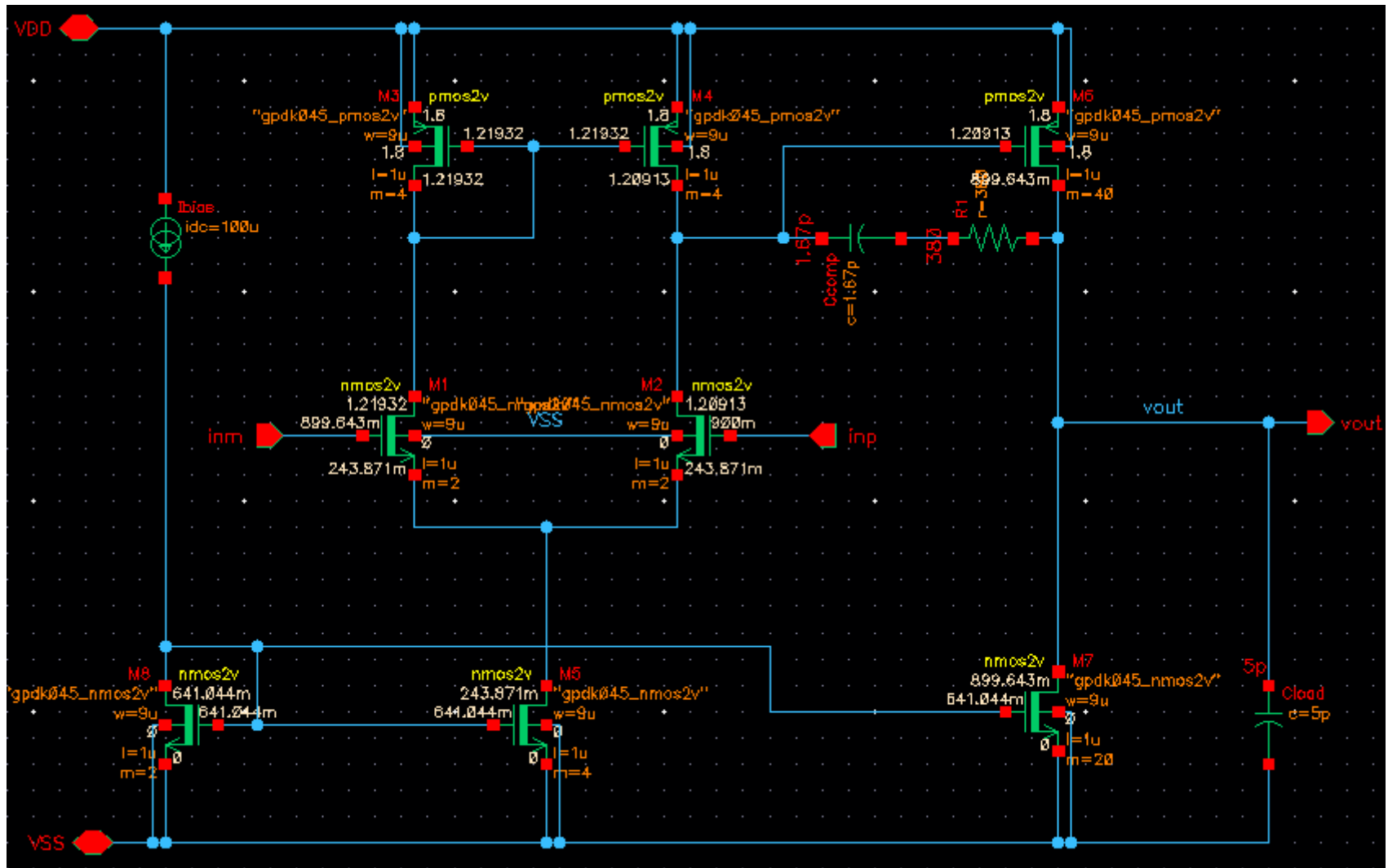


# DC Operating Points

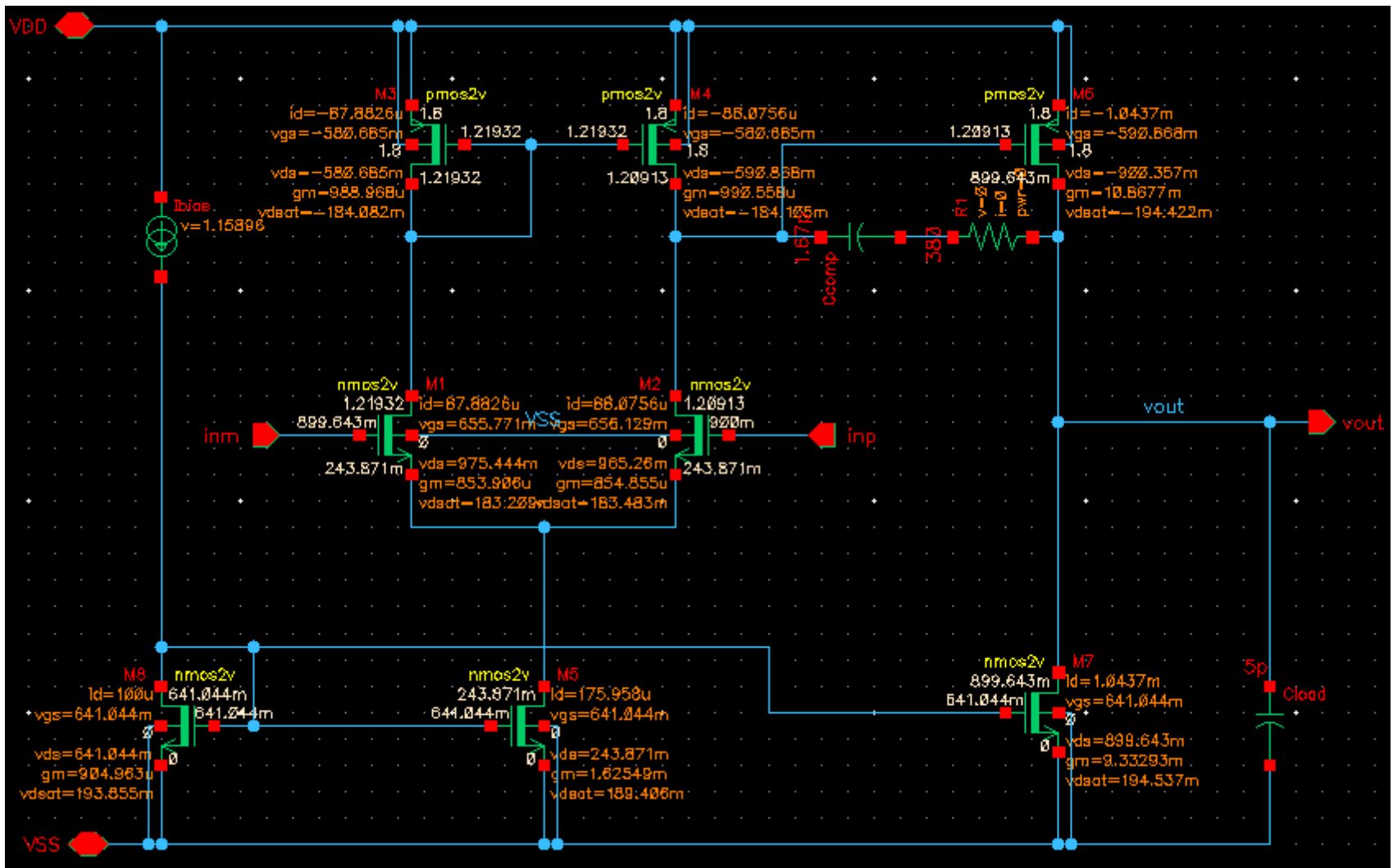

# AC simulation

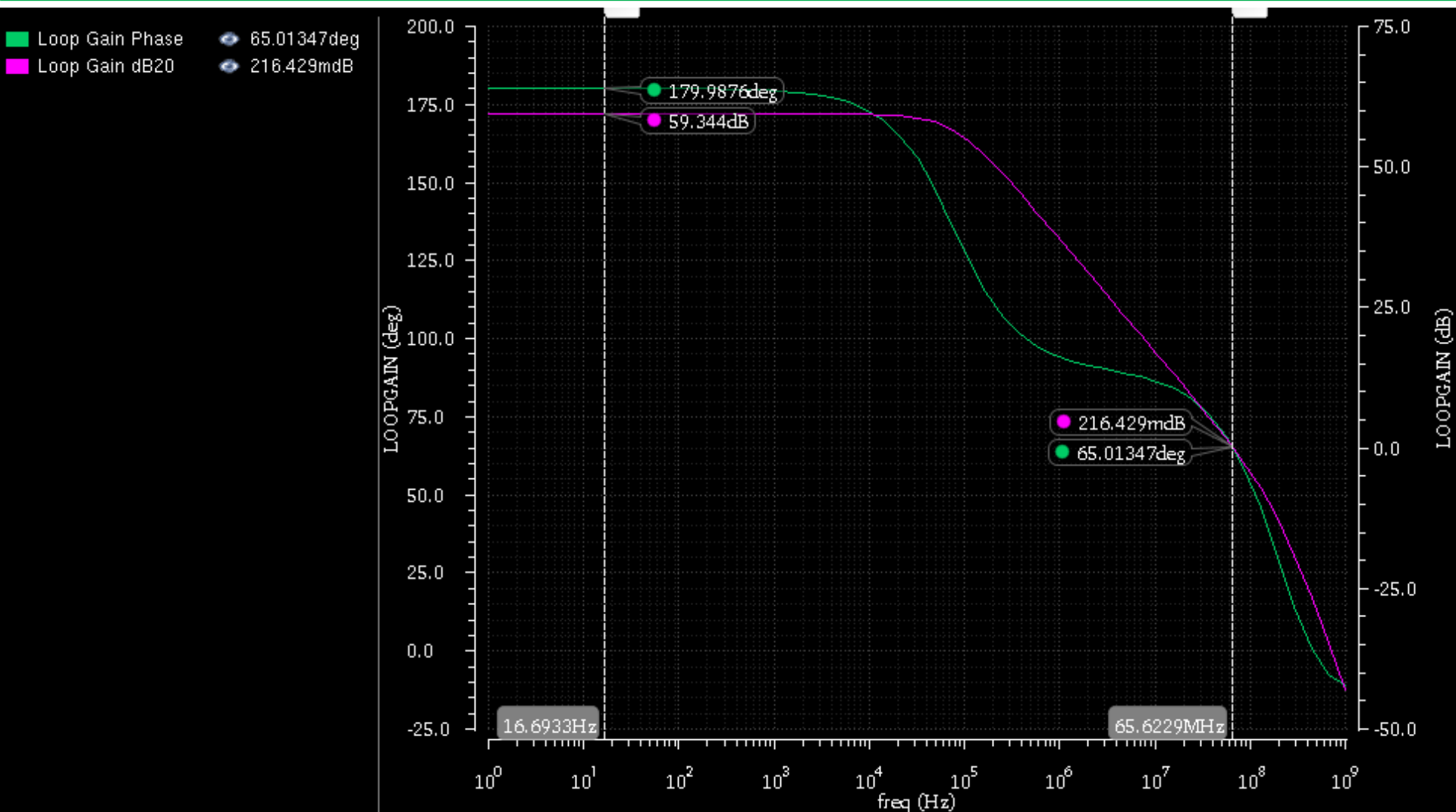

# New Size

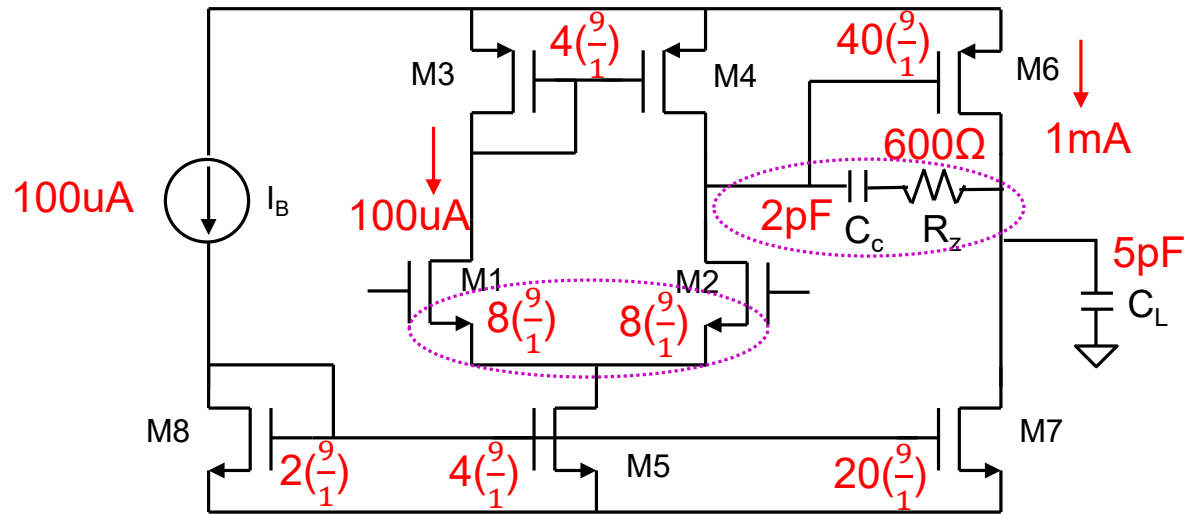

To achieve  $f_u = 100MHz$  from  $65MHz$  in simulation, increase  $gm_1$

1. Simulate with a new size and check  $f_u$  and PM

$$(\frac{W}{L})_1 = 2(\frac{9}{1}) \rightarrow (\frac{W}{L})_1 = 8(\frac{9}{1})$$


2. If the PM is low, increase  $C_c$

$$C_c = 1.6 pF \rightarrow C_c = 2 pF$$


3. Adjust  $R_z$  up or down to see if you can get an optimum response

$$R_z = 380 \Omega \rightarrow R_z = 600 \Omega$$


## Schematic with New Size

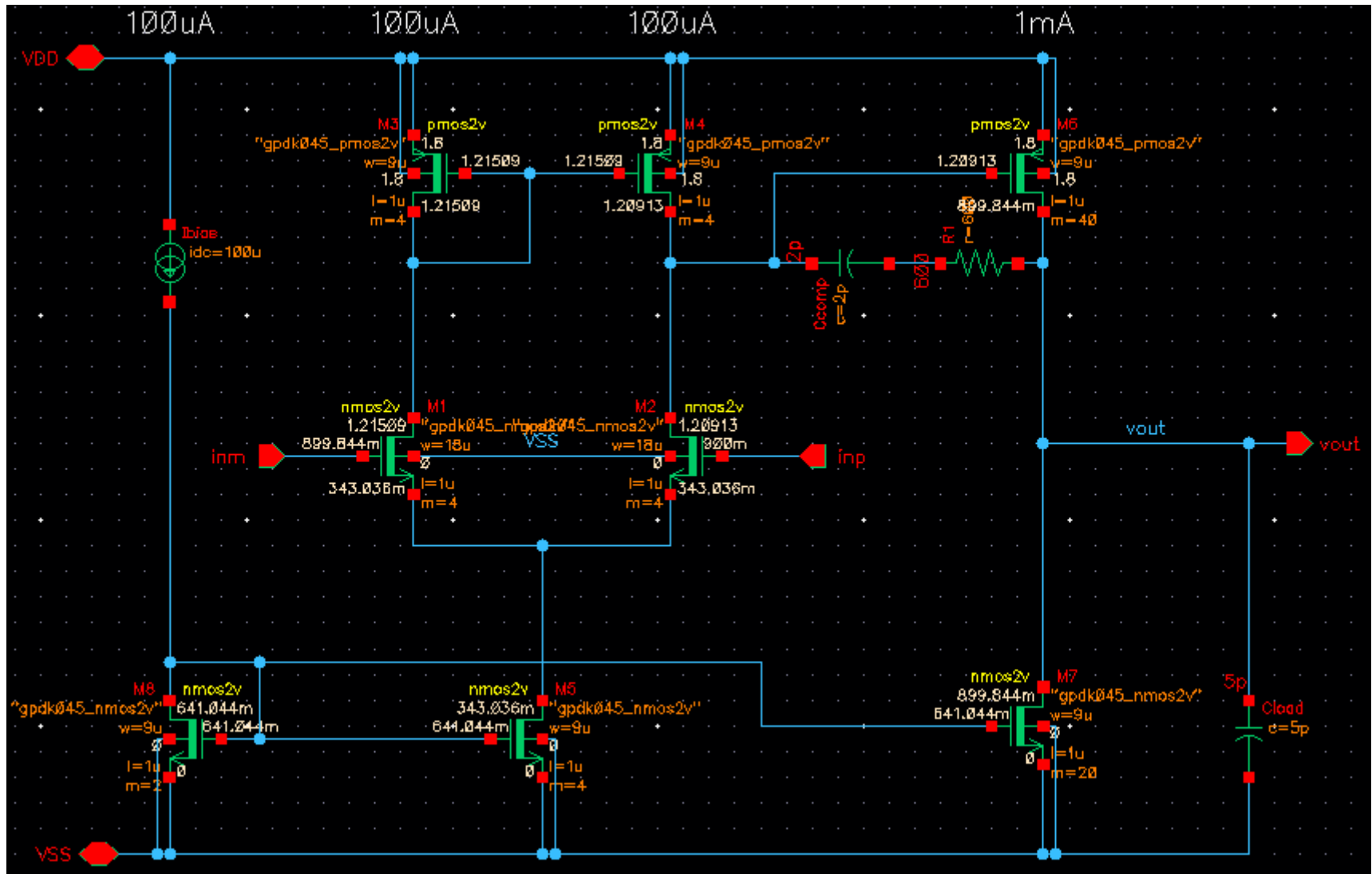

# DC Operating Points

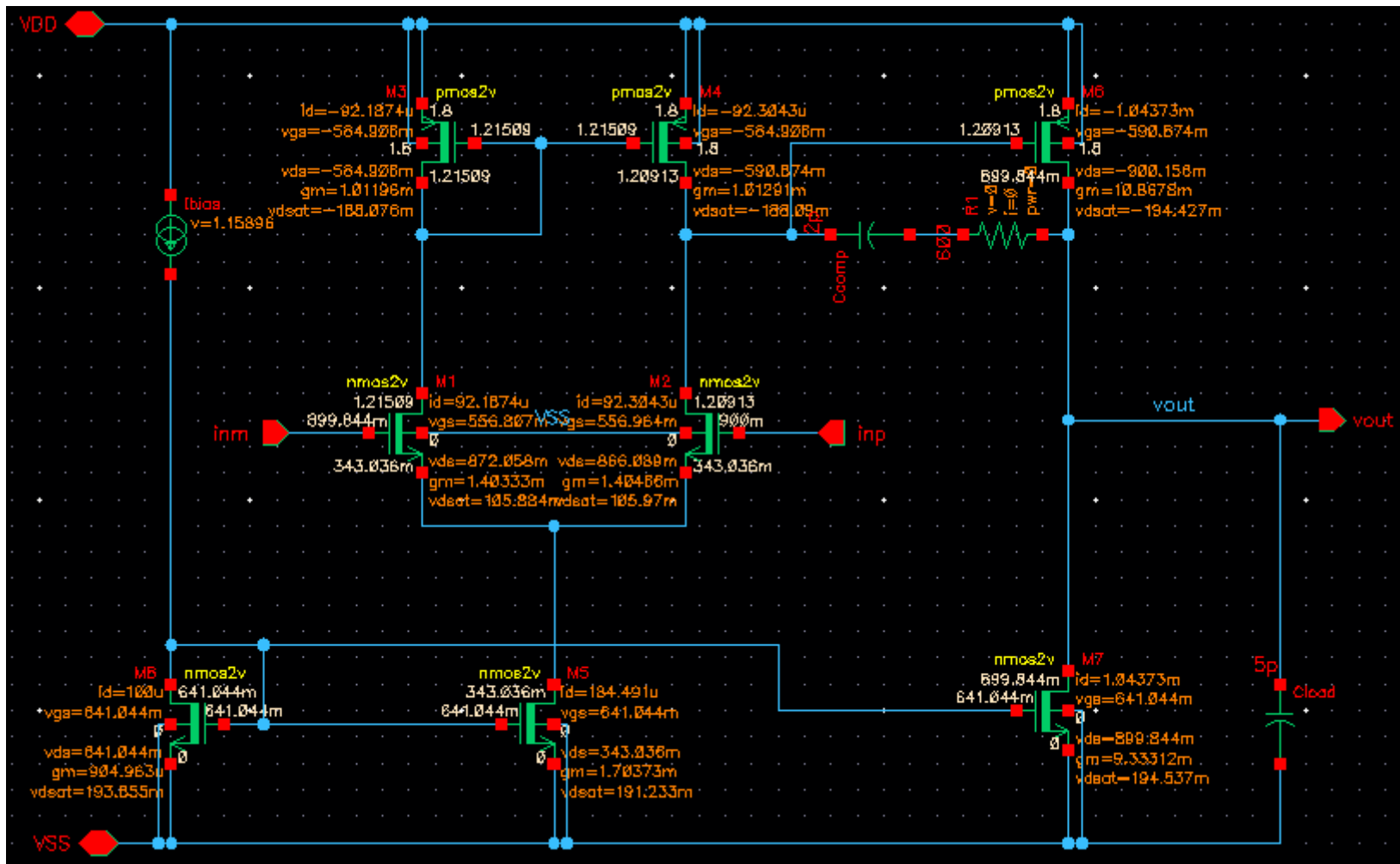


# AC simulation

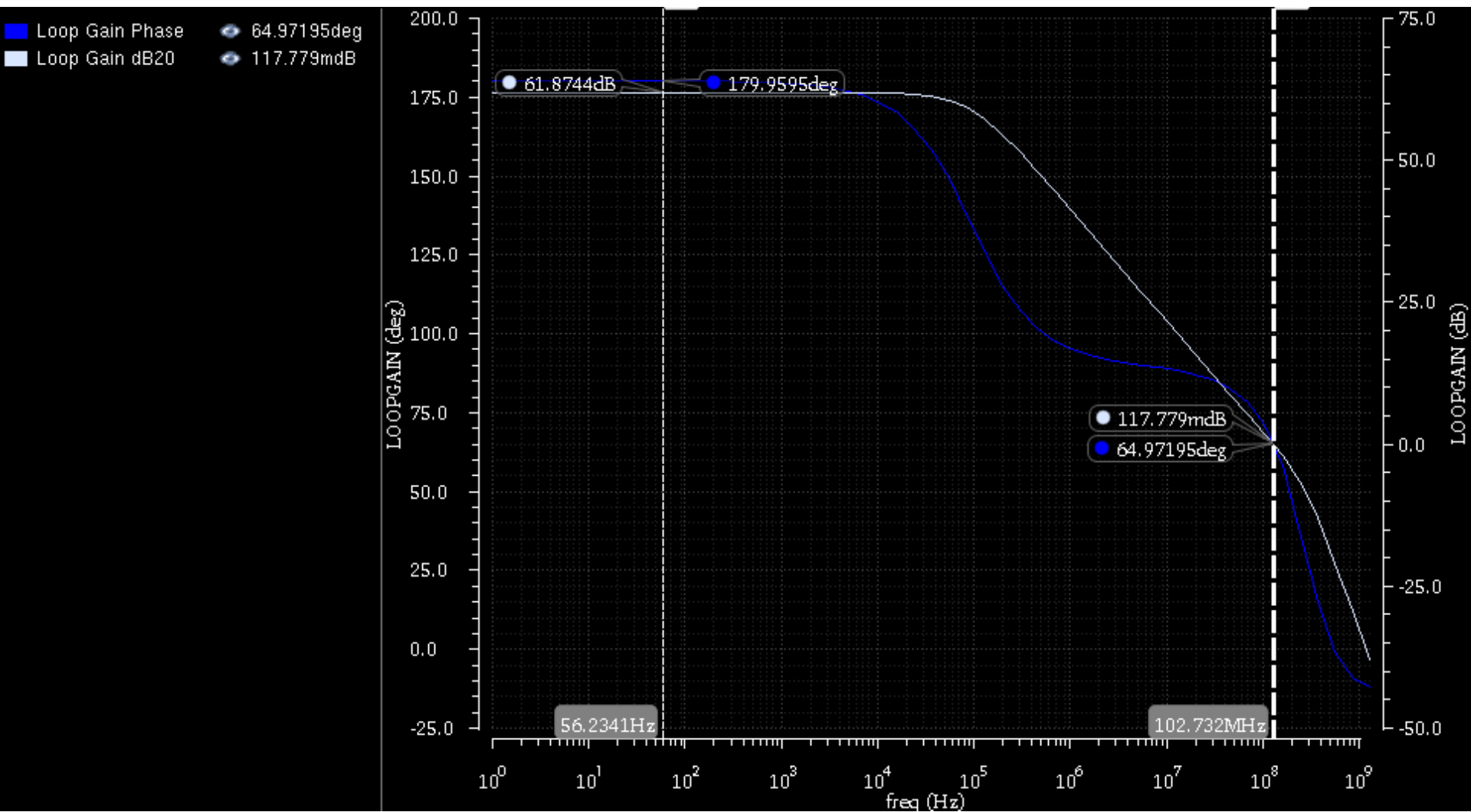



# Transient Simulation for 10mV Pulse

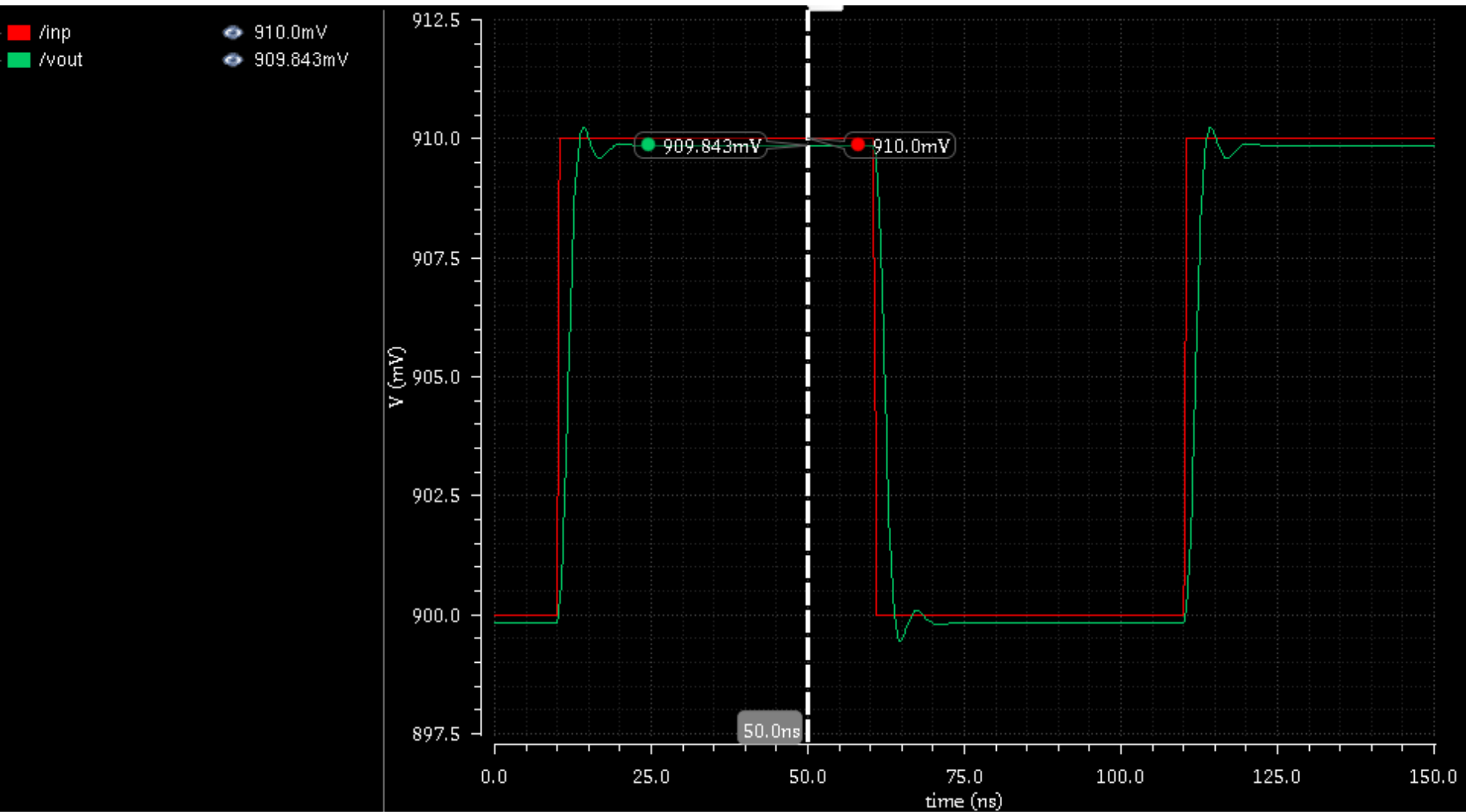

# Transient Simulation for 500mV Pulse

