 


Transistor Sizing

Lecture 5

Advanced Digital IC Design

Khosrow Ghadiri





- Rule: Select W/L ratio to provide the gate with same current-driving capability in both directions equal to that of basic inverter
- Basic inverter $\left\{ \begin{array}{l} \left(\frac{W}{L}\right)_n = n \quad \text{typically } n = 1 \\ \left(\frac{W}{L}\right)_p = p \quad \text{typically } p = 1.5 \end{array} \right.$
- For match design $\frac{p}{n} = \frac{\mu_n}{\mu_p}$ typical $p = 2n$ and for minimum area $p = n$



- Network Equivalent W/L ratio:
- Rational :

$$R_{on} = \frac{\text{Constant}}{\frac{W}{L}}$$

- Transistor Series Connection

$$R_{series} = R_{on1} + R_{on2} + \dots = \frac{\text{Constant}}{\left(\frac{W}{L}\right)_1} + \frac{\text{Constant}}{\left(\frac{W}{L}\right)_2} + \dots$$

$$R_{series} = \text{Constant} \left[\frac{1}{\left(\frac{W}{L}\right)_1} + \frac{1}{\left(\frac{W}{L}\right)_2} + \dots \right] = \frac{\text{Constant}}{\left(\frac{W}{L}\right)_{eq}}$$



- Network Equivalent W/L ratio:


$$\left(\frac{W}{L}\right)_{eq} = \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_1} + \frac{1}{\left(\frac{W}{L}\right)_2} + \dots} \quad \text{Transistor series connection}$$

$$\left(\frac{W}{L}\right)_{eq} = \left(\frac{W}{L}\right)_1 + \left(\frac{W}{L}\right)_2 + \dots \quad \text{Transistor parallel connection}$$



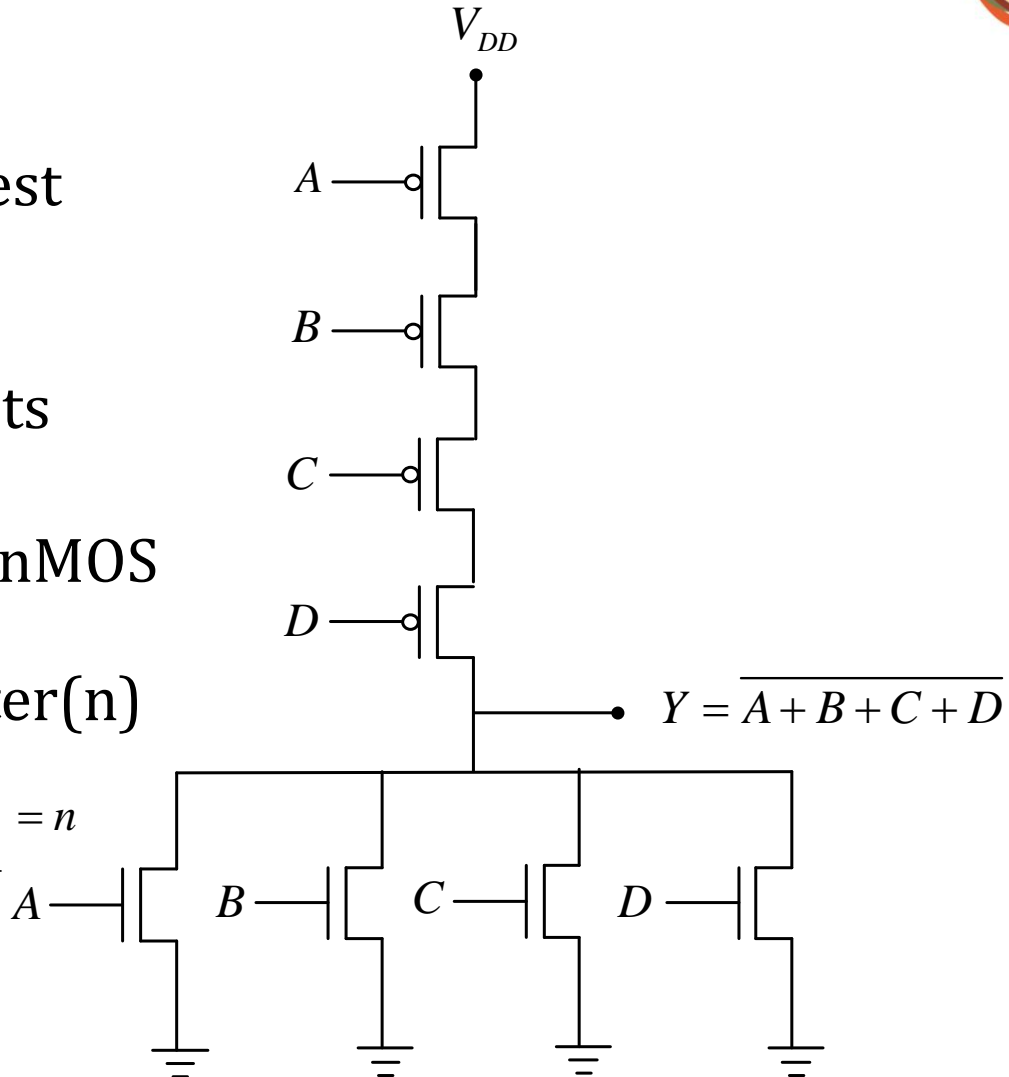
- Example
- **Four-input Nor Gate**
- Worst case(The lowest current) for PDN
- Only one of nMOS transistor is on(inputs high)
- Select the $\frac{W}{L}$ of each nMOS equal to that of the nMOS of basic inverter(n)


$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = n$$





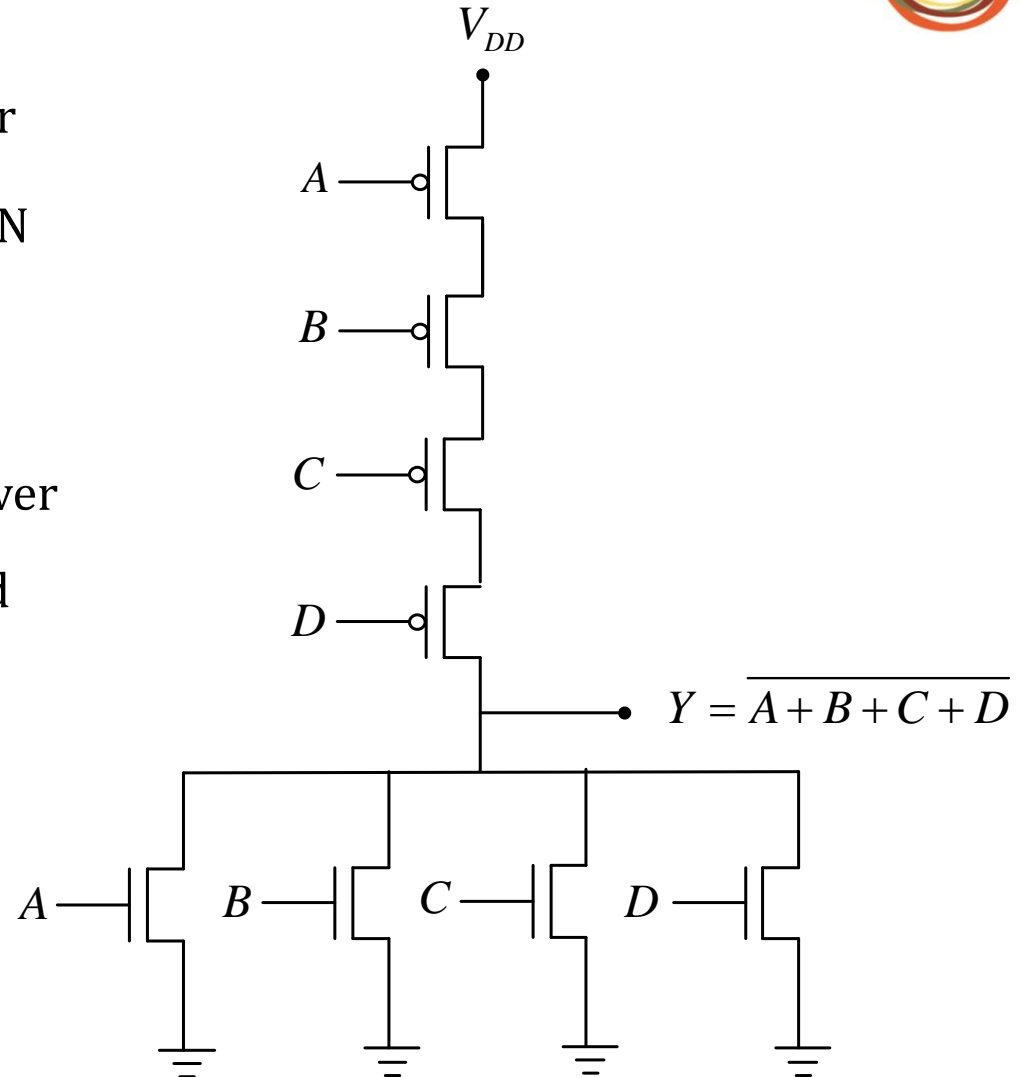- Example
- **Four-input Nor Gate**
- Worst Case (stacked pMOS) for PUN
- Four series pMOS transistor ON (inputs low)
- Select the $\frac{W}{L}$ of each pMOS transistor equal to 4 times of pMOS of basic inverter(4p)
- Note: pMOS devices have a lower mobility relative to nMOS devices. Stacking pMOS should be avoided.
- (NAND implementation preferred over a NOR implementation for implementing generic logic.)



 

- Short channel velocity saturation


$$1 \frac{V}{\mu m} < \text{typical } E_{cr} < 5 \frac{V}{\mu m}$$

$$E_{cr} = \frac{V_{DS}(v_{sat})}{L}$$

$$v_{sat} = \mu_n \frac{V_{DS}(v_{sat})}{L}$$


$$V_{DS}(v_{sat}) = \frac{L}{\mu_n} v_{sat}$$

$$v_{sat} = 10^7 \text{ cm/s}$$

 



- I_{DS} vs. V_{DS} Characteristic

 



- Ids vs. Vds Characteristic

$$I_{DS}(\text{resistive}) = \mu_n C_{ox} \frac{W}{L} v_{DS} \left[(V_{GS} - V_T) - \frac{1}{2} V_{DS} \right]$$

$$V_{DS} = V_{OV} = V_{GS} - V_T \text{ for } I_{DS}(\text{sat})$$

$$I_{DS}(\text{Edge of Sat}) = \mu_n C_{ox} \frac{W}{L} V_{DS}(\text{sat}) \left[V_{GS} - V_T - \frac{1}{2} V_{DS}(\text{sat}) \right]$$

$$V_{ov} > V_{DS}(\text{sat})$$


$$I_{DS}(\text{Edge of Sat}) = \mu_n C_{ox} \frac{W}{L} V_{DS}(\text{sat}) \left[V_{GS} - V_T - \frac{1}{2} V_{DS}(\text{sat}) \right]$$

$$I_{DS}(\text{Edge of Sat}) = C_{ox} W v_{sat} \left[V_{GS} - V_T - \frac{1}{2} V_{DS}(\text{sat}) \right]$$

$$I_{DS}(\text{Sat}) = \mu_n C_{ox} \frac{W}{L} v_{D}(\text{sat}) \left[V_{GS} - V_T - \frac{1}{2} V_{DS}(\text{sat}) \right] (1 + \lambda V_{DS})$$




- I_{DS} vs. V_{DS} Characteristic

 



- Ids vs. Vgs Characteristic

 



- Effects of Fan-in and Fan-out on propagation delay.
- Observation: Each additional input to CMOS gate requires two additional transistor, one nMOS and one pMOS.
 - Increase chip area
 - Increase the total effective capacitance per gate
 - Increase propagation delay
- Fan-in limited to 4



- Special need Alternatives
- **1 Pseudo – nMOS logic**
- Replace PUN in a CMOS by a single permanently on pMOS transistor
- Advantage: Reduction in transistor count(area)
- Disadvantage: static power dissipation V_{OL} dependence on the $\frac{W}{L}$ ratio.
- **2 Pass transistor logic(PTL)**
- MOS transistor as switch in the series path from input to output.
- Disadvantage: Signal level degradation.



- Special need Alternatives
- **3** ECL Emitter Coupled Transistor
- Bipolar logic circuit.

$$\frac{W}{L}$$

$$V_{OL}$$



- Summary of the implication of scaling the device dimension by a factor $\frac{1}{s}$ where $s > 1$

Parameters	Scaling	Parameters
W, L, t_{ox}	$1/s$	
V_{DD}, V_T	$1/s$	
<i>Area</i>	$1/s^2$	WL
C_{ox}	s	ϵ_{ox} / t_{ox}
k'_n, k'_p	s	$k'_n = \mu_n C_{ox}, k'_p = \mu_p C_{ox}$
C_{gate}	$1/s$	WLC_{ox}
t_p (intrinsic)	s	$\alpha C / k' V_{DD}$
<i>Energy</i>	$1/s$	CV_{DD}^2
P_{dyn}	$1/s^2$	$f_{max} CV_{DD}^2 = CV_{DD}^2 / 2t_p$
<i>Power density</i>	1	$P_{dyn} / \text{device area}$



- Note: V_{DD} may not follow the scaling factor

$$V_{DD} = 5V \quad 0.5\mu m \text{ process}$$

$$V_{DD} = 1.2V \quad 0.13\mu m \text{ process}$$

- Note: V_T is not decreased with the same factor.